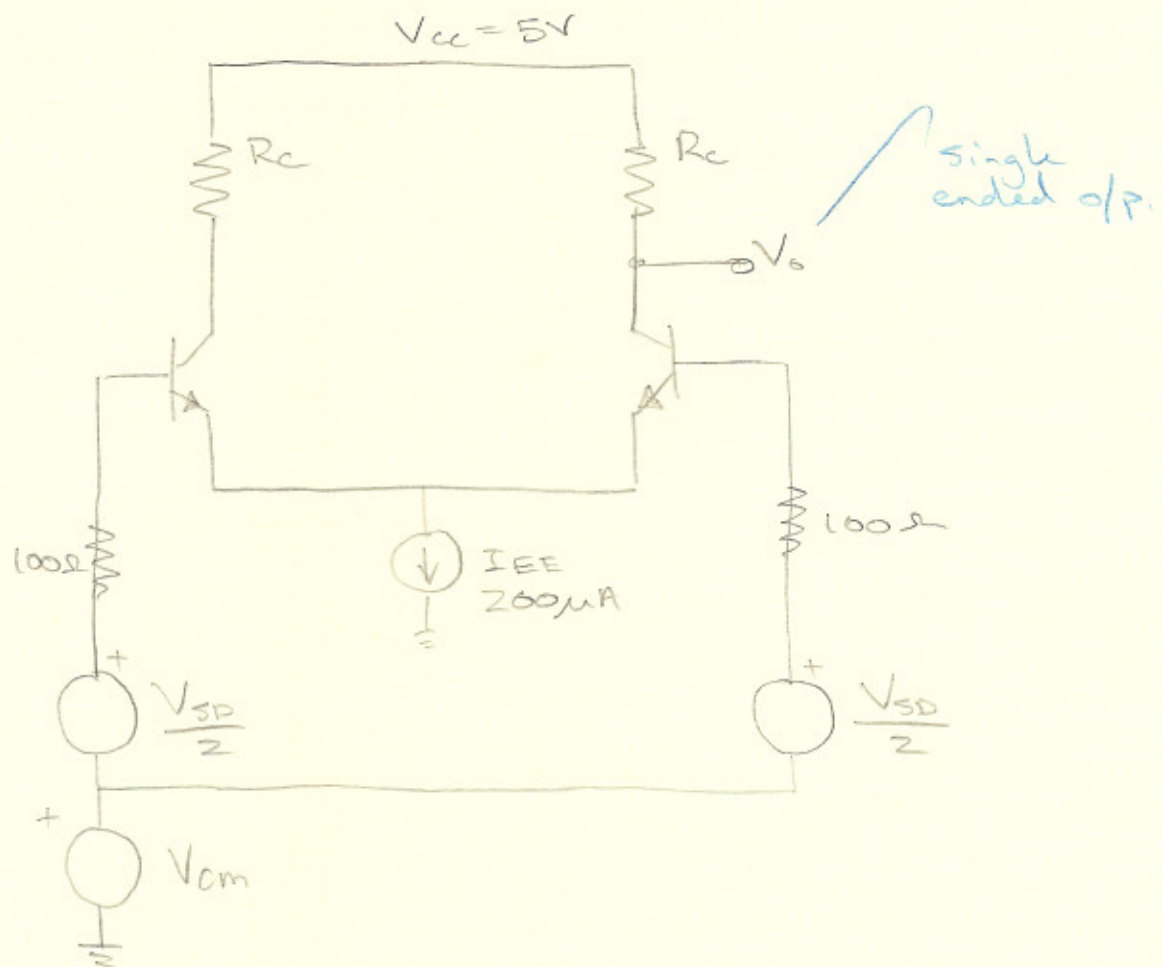



DP 8.103

A.  $A_{dm} = 100$  B.  $V_{cmmax} = ?$



A.

Differential mode Small Signal Circuit

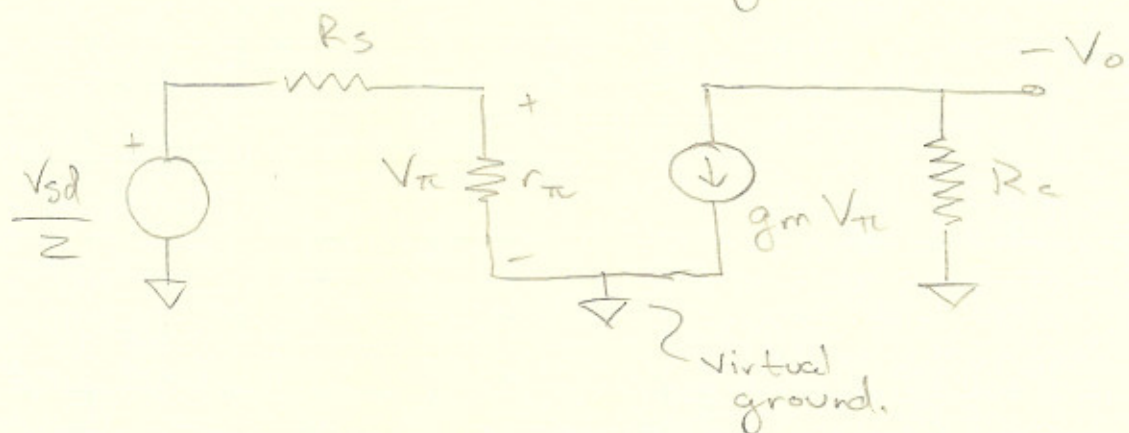

$$A_{dm} = \frac{V_o}{V_{sd}}$$


$$-V_o = -g_m V_{\pi} R_c$$

$$V_o = g_m \left( \frac{r_{\pi}}{r_{\pi} + R_s} \right) V_{sd} \cdot \frac{1}{2} R_c$$

$$A_{dm} = \frac{\beta R_c}{(R_s + r_{\pi})^2} = 100$$


$$\therefore R_c = 52 \text{ k}\Omega$$

B.

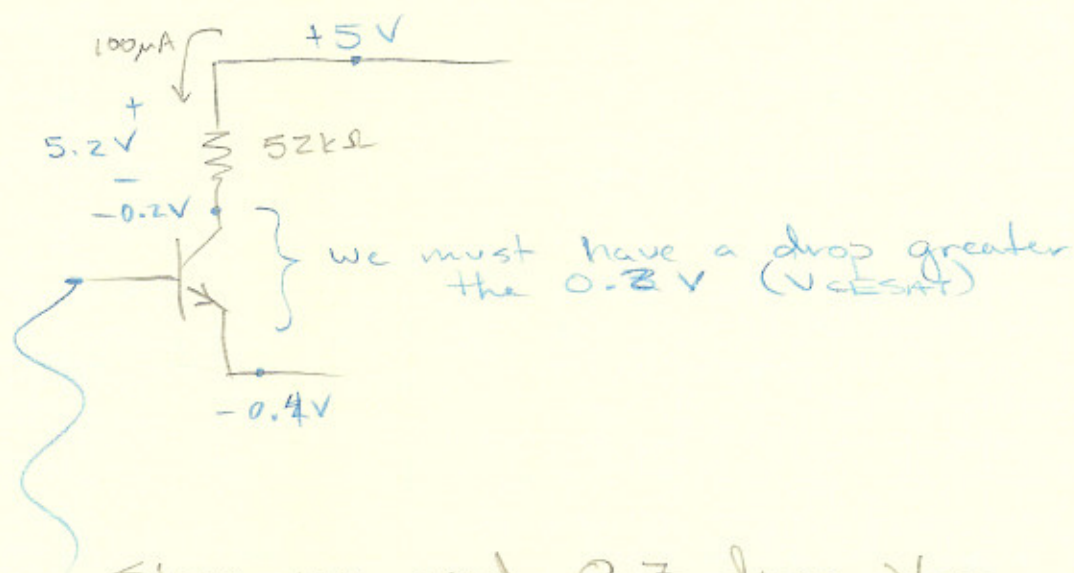


Since we need 0.7 drop  $V_{BE}$   
 $V_{B \max} < 0.3V$

# Operational Amplifier

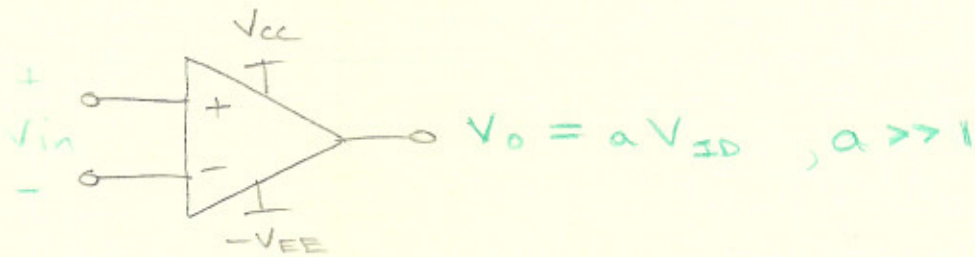


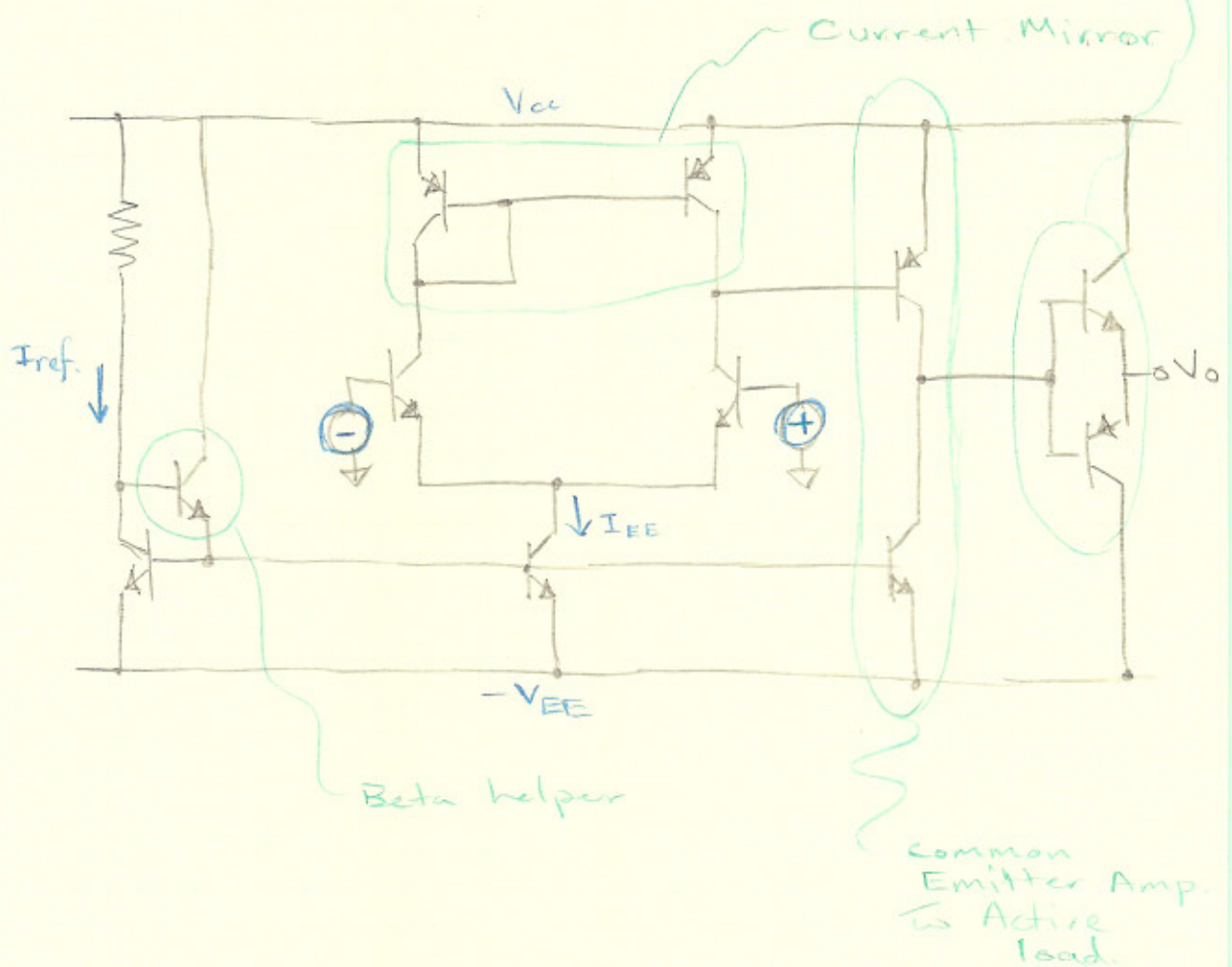note: In practice: 2 gain stages  
Use active loads class B Amp.






## Finite Gain

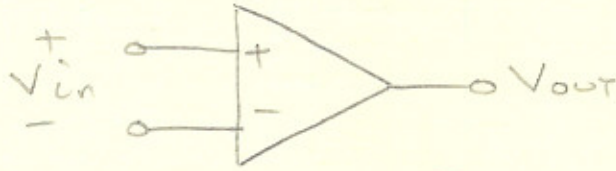


$$V_{out} = a V_{in} \quad \text{amp gain.}$$

Non inverting configuration

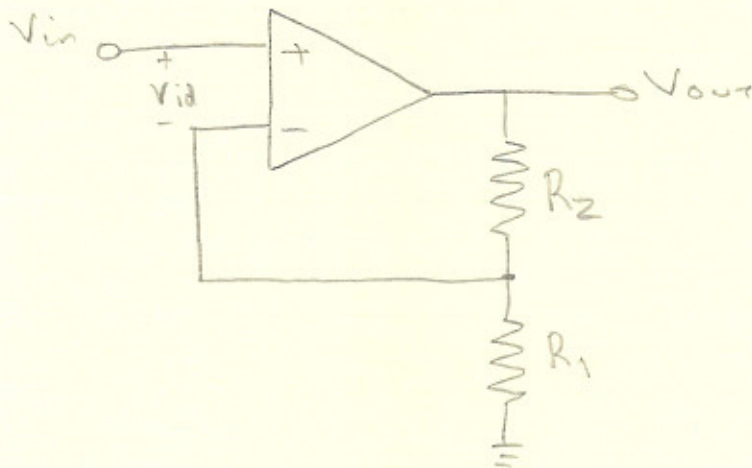

$$V_o(V_i) = ?$$

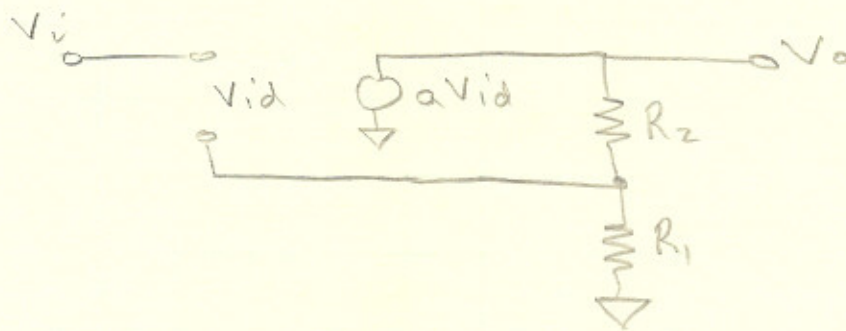

$$V_{id} = V_i - V_o \frac{R_2}{R_1 + R_2}$$

$$V_{id} = \frac{V_o}{a}$$


$$\frac{V_o}{a} = V_i - V_o \frac{R_2}{R_1 + R_2}$$

$$V_o \left( \frac{1}{a} + \frac{R_2}{R_1 + R_2} \right) = V_i$$

$$\frac{V_o}{V_i} = \frac{1}{\frac{1}{a} + \frac{R_2}{R_1 + R_2}}$$

as  $a \rightarrow \infty$
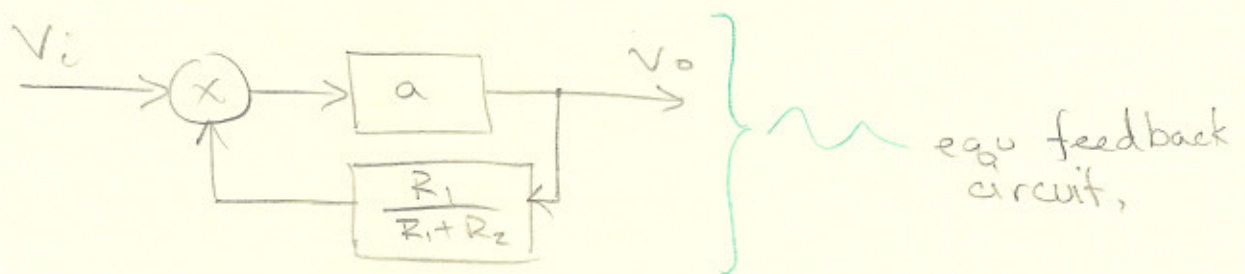
$$\frac{V_o}{V_i} = 1 + \frac{R_2}{R_1} \quad \left. \vphantom{\frac{V_o}{V_i}} \right\} \text{commonly known eqn.}$$



How do we solve the circuit assuming  $a \rightarrow \infty$

### Rules

- \* Make Sure that there is negative feedback.
- \* The op amp will  $V_{id} = 0$
- \* OP AMP i/p's take no current