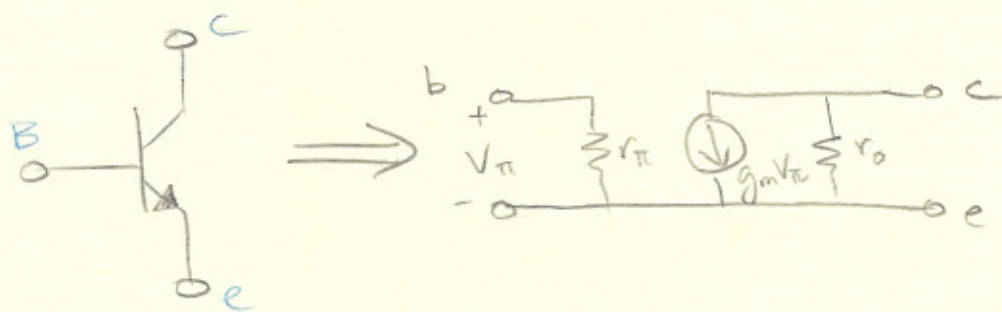


Capacitors behave like short circuit to the signal.

We use small signal analysis to study pathways.



This is valid for active region

$$g_m = \frac{I_c}{V_T} \quad r_{\pi} = \frac{\beta}{g_m} \quad r_o = \frac{V_A}{I_c}$$

$V_T$ : thermal voltage

$$V_T = \frac{kT}{q} \quad \left\{ \begin{array}{l} k: \text{boltzman constant} \\ T: \text{absolute temp.} \\ q: \text{electron charge} \end{array} \right.$$

$$V_T \sim 0.026 \text{ V} @ 300^\circ \text{K}$$

$V_A$ : early Voltage

Other considerations for small signal analysis


\* Constant independent sources are set to zero

$$V_S \rightarrow SC$$


$$C_S \rightarrow OC$$

\* For now caps are short circuit.

\* Other components stay

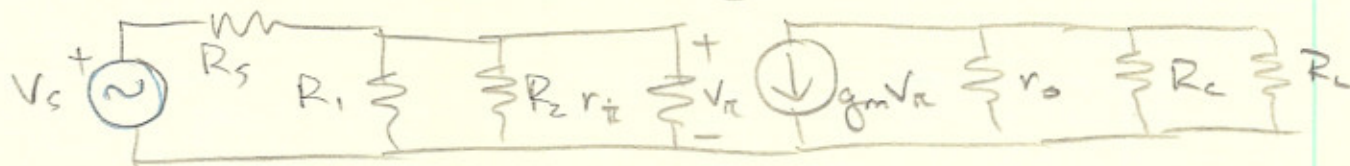

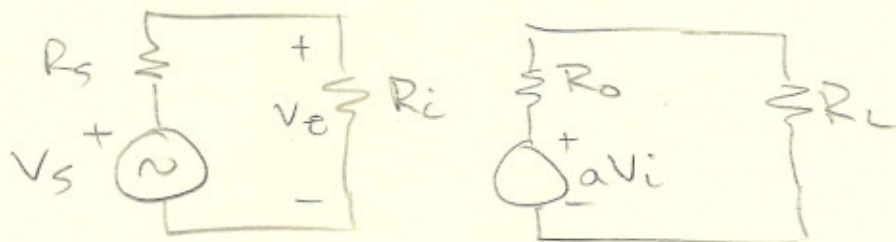Now we can find the model for the whole thing



note for bias point quantities we use upper case for ~~large~~ signal analysis and lower case for small signal analysis

Input Resistance: ( $R_i$ ) Usually the  $R_i$  value is the thevin value. We can see this from inspection of the circuit.

Output Resistance: ( $R_o$ ) Passive i/p source  $V_{\pi} = 0 \therefore g_m V_{\pi} = 0$ . Then we apply a test source ...  $R_o = R_c // r_o$

Voltage gain:

$$a_v = \frac{V_o}{V_i}$$