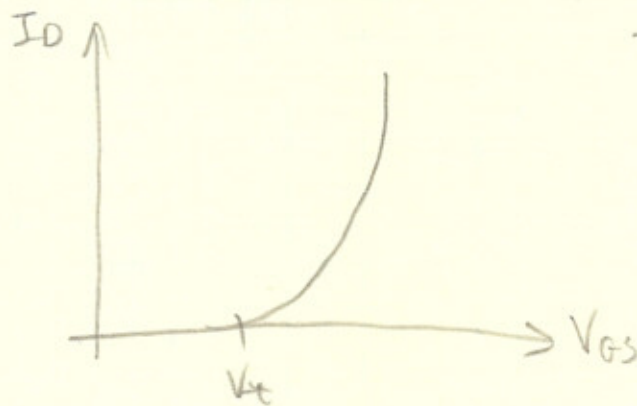
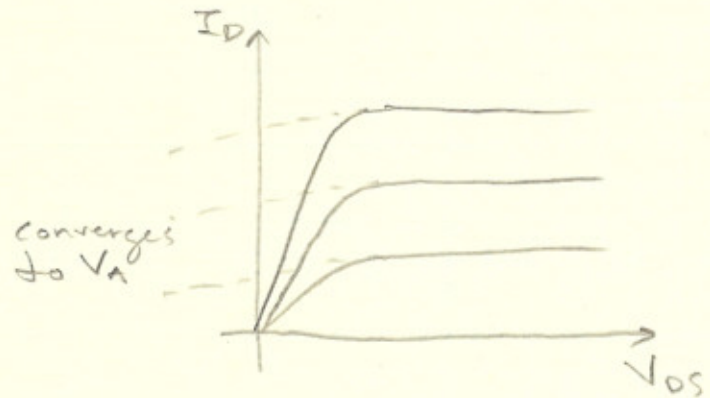
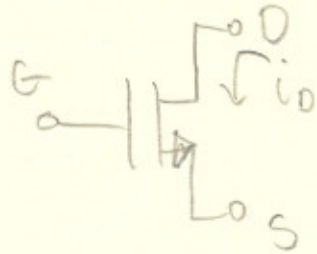


MOS FET Equations

CUTOFF:  $I_D = 0$   $V_{GS} < V_t$

TRIODE:  $I_D = K [2(V_{GS} - V_t)V_{DS} - V_{DS}^2]$

$$V_{DS} < V_{GS} - V_t$$


ACTIVE:  $I_D = K (V_{GS} - V_t)^2$

$$V_{DS} \geq V_{GS} - V_t$$

For output resistance

$$\lambda = \frac{1}{V_A}$$


## Small signal

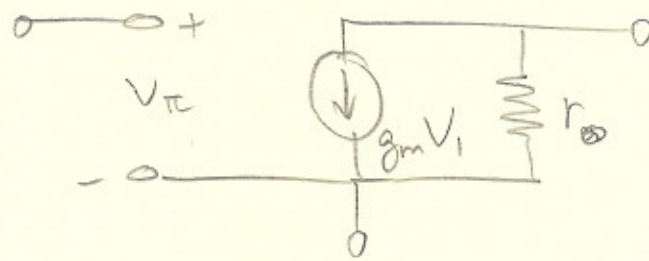

$$g_m = \frac{\partial I_s}{\partial V_{gs}}$$

$$r_o = \frac{\partial I_o}{\partial V_{ds}}$$

## Current Source

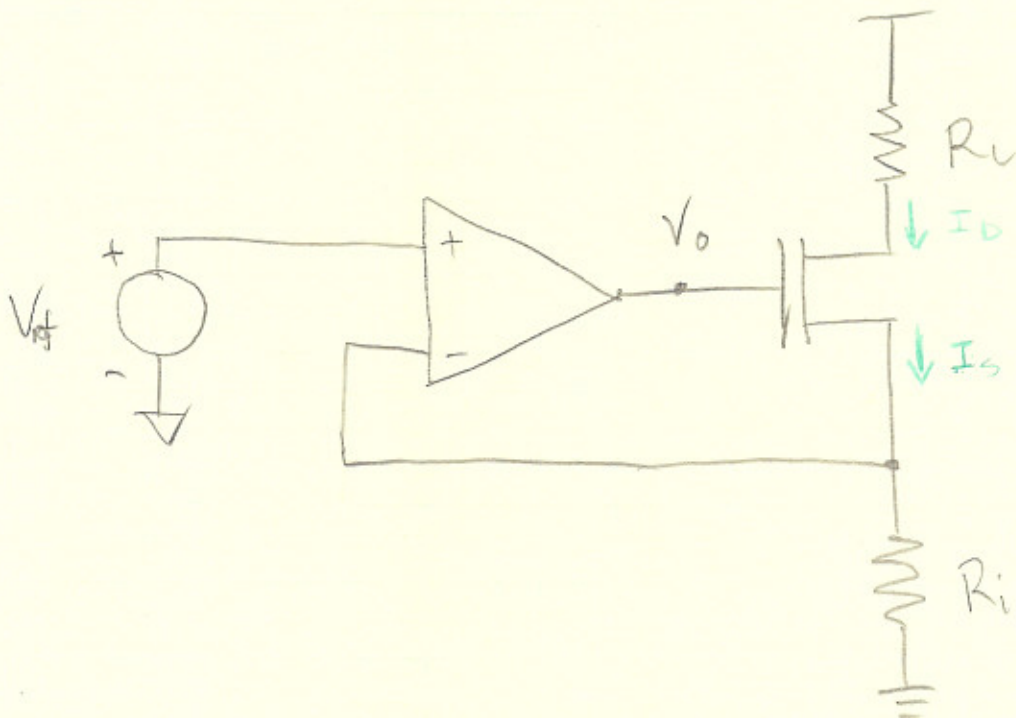

$$I_S = \frac{V_{ref}}{R_1} \Rightarrow I_D$$

$$I_D = I_D = K(V_{GS} - V_t)^2$$


$$V_{GS} = V_{OA} - V_{ref}$$

$$\frac{V_{ref}}{R_1} = K(V_{GS} - V_t)^2$$


$$\frac{V_{ref}}{R_1} = K(V_{OA} - V_{ref} - V_t)^2$$

$$V_{OA} = V_{ref} + V_t \pm \sqrt{\frac{V_{ref}}{KR_1}}$$


## Voltage Regulators

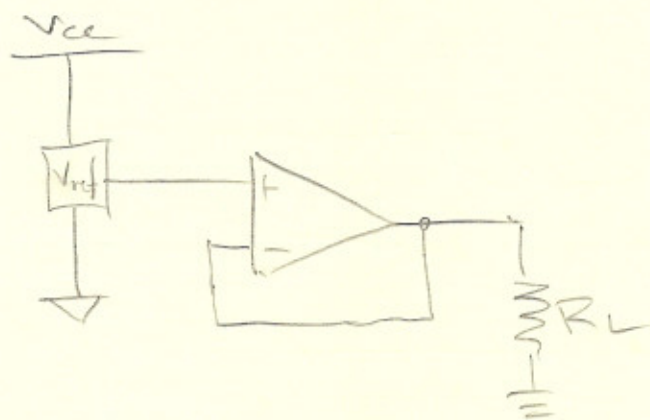

When the load requires more current.

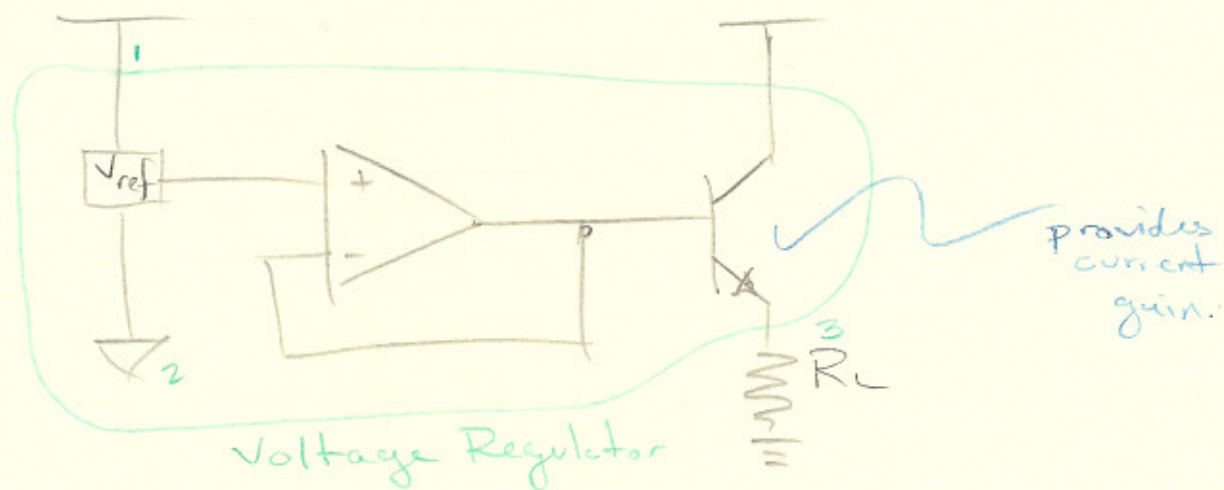


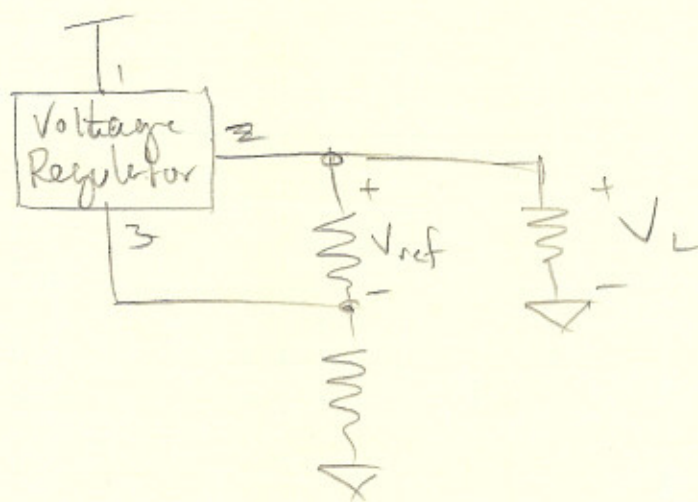Adjustable Voltage divider ( $V_{out} > V_{ref}$ )






## Comparator

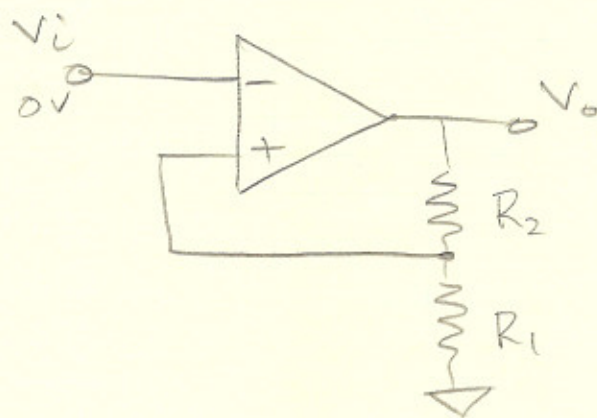

$$V^+ = V_{cc} \frac{R_1}{R_2 + R_1} > 0$$

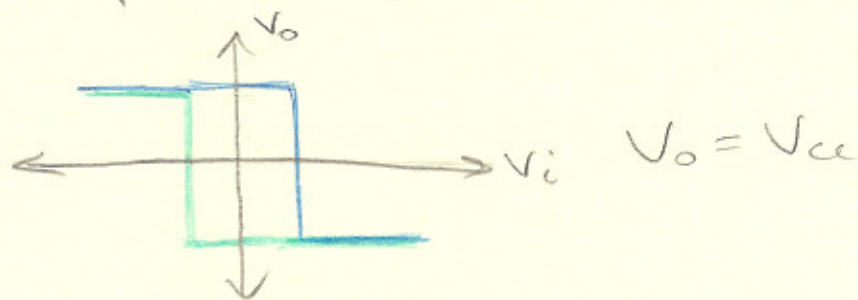then the circuit is saturated positive there is positive feedback.




if  $V_i$  is increased until it reaches

$$V_i = V^- > V^+$$

then the output becomes  $-V_{cc}$ ; It will stay this way until

$$V_i = V^- < V^+ = -V_{cc} \frac{R_1}{R_2 + R_1}$$

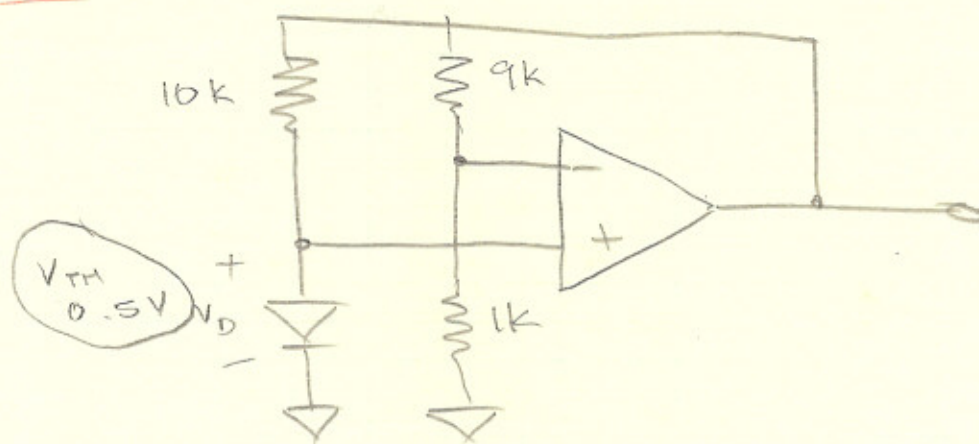EX:

Find the stable equilibrium points.

Suppose

$$V_o = -V_{cc} \begin{cases} V^- = -\frac{V_{cc}}{10} \\ V^+ = -V_{cc} \end{cases}$$

$$V_{ID} = -V_{cc} + \frac{V_{cc}}{10} = -\frac{9}{10}V_{cc} < 0$$

Therefore the output will stay at  $V_{cc}$

$$V_o = +V_{cc} \begin{cases} V^- = \frac{V_{cc}}{10} \\ V^+ = 0.5V \end{cases}$$

$$V_{ID} = V^+ - V^-$$

$$= 0.5V - \frac{V_{cc}}{10} < 0$$


$\therefore V_o = +V_{cc}$  is not stable

However, the system does have an equilibrium point at

$$V_{ID} = 0 = 0.5V - \frac{V_o}{10}$$

$$V_o = 5V$$

Stable ?

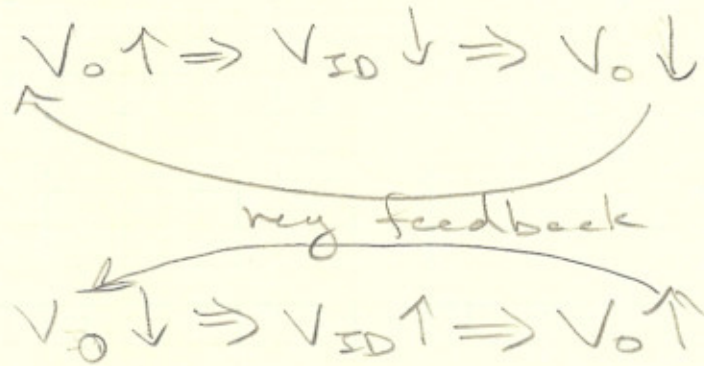

This holds true until the diode goes in reverse bias

$$0 < V_o \leq 0.5V$$

$$V_o = V^+$$

$$V^- = V_o \frac{1}{10}$$

$$V_{ID} = V_o - V_o \frac{1}{10}$$

$\therefore V_o$  will go to  $V_{cc}$  but stop at  $V_o = 5V$ .