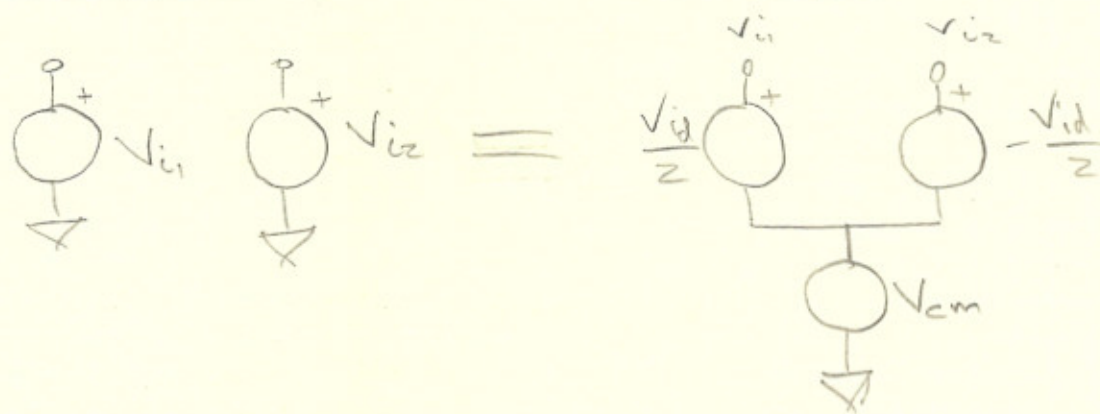


Assignment # 3: 8.91, 8.101, 8.104, 8.126

Differential and Common Modes



$$V_{i1} = \frac{V_{id}}{2} + V_{cm}$$

$$V_{i2} = -\frac{V_{id}}{2} + V_{cm}$$


$$V_{id} = V_{i1} - V_{i2}$$

$$V_{cm} = \frac{V_{i1} + V_{i2}}{2}$$

V_{id} = Differential-Mode Voltage

V_{cm} = Common-Mode Voltage.

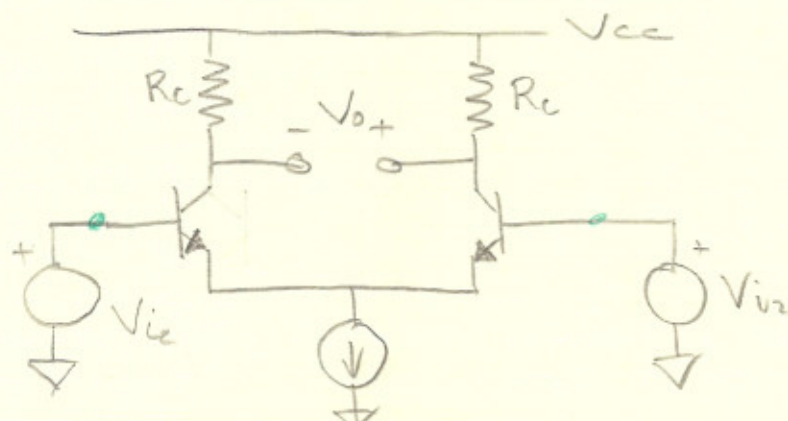Bipolar T. implementation of a differential Amp



... 1 input.


$$Q_1 = Q_2$$

* Bias Calculation

Assume:

$$V_{cm} = 0$$

$$V_{id} = 0$$

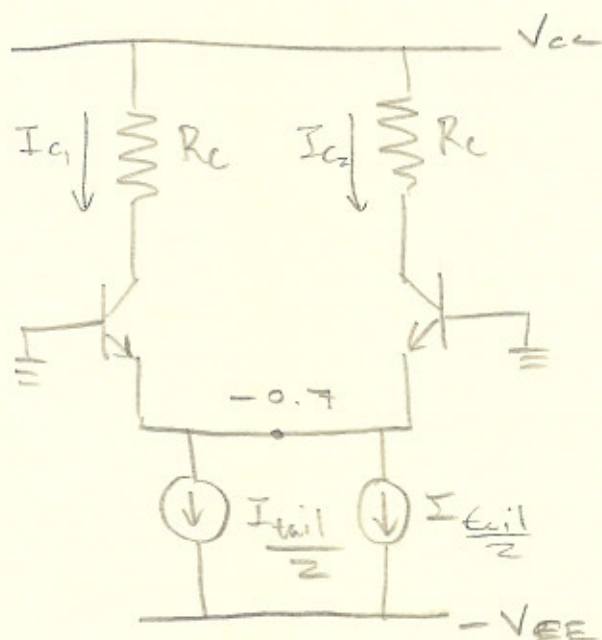

$$I_{c1} = I_{c2}$$


$$V_{c1} = V_{cc} - \frac{I_{tail}}{2} R_{c1}$$

$$= V_{cc} - I_c R_{c1}$$

$$V_{CE1} = V_{c1} - V_{E1} = V_{c1} + 0.7V$$


$$V_{CE1} \geq V_{CESAT} \text{ for FA region}$$

EX

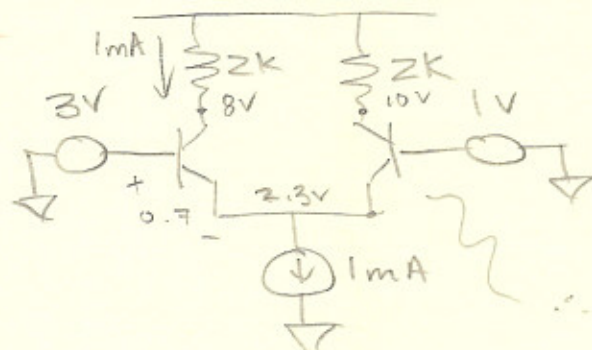

∴ this transistor is in cut off

* Small signal analysis.

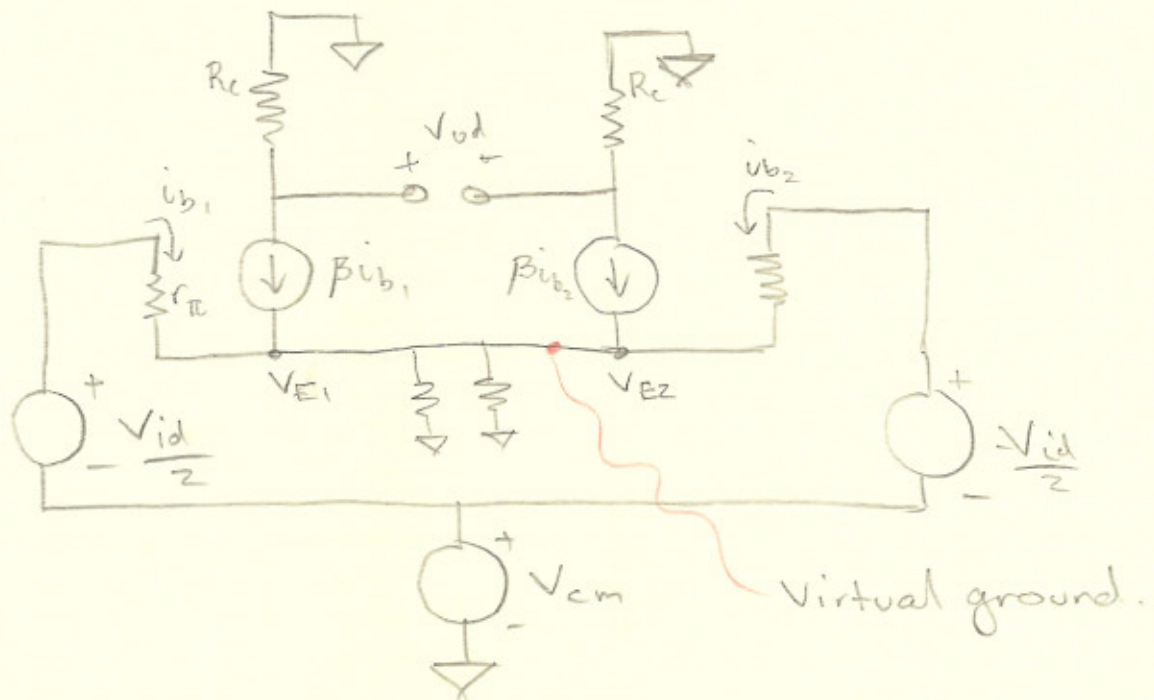


This is a linear circuit, hence superposition applies; We can analysis differential and common mode separately.

Assuming $V_{cm}=0$; $V_{id} > 0$

$$\left. \begin{aligned} V_{E1} &= -V_{E2} \\ V_{O1} &= -V_{O2} \\ i_{b1} &= -i_{b2} \end{aligned} \right\} \text{b/c of sym}$$

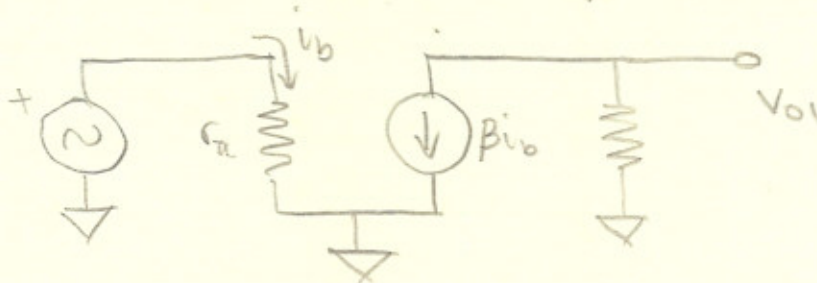\therefore we can solve half the circuit.



$$V_{od} = V_{o1} - V_{o2} = 2V_{o1}$$

a_{dm} : differential mode gain

$$a_{dm} = \frac{V_{od}}{V_{id}}$$

$$a_{dm} = \frac{2V_{o1}}{V_{id}}$$


$$\frac{V_{o1}}{V_{id}} = \frac{-g_m R_c}{2}$$

$$\therefore a_{dm} = -g_m R_c$$

Now Assuming $V_{cm} > 0$; $V_{id} = 0$

$$\left. \begin{array}{l} V_{o1} = V_{o2} \\ i_{b1} = i_{b2} \\ V_{e1} = V_{e2} \end{array} \right\} \text{ b/c of sym.}$$

Analyse One half circuit.

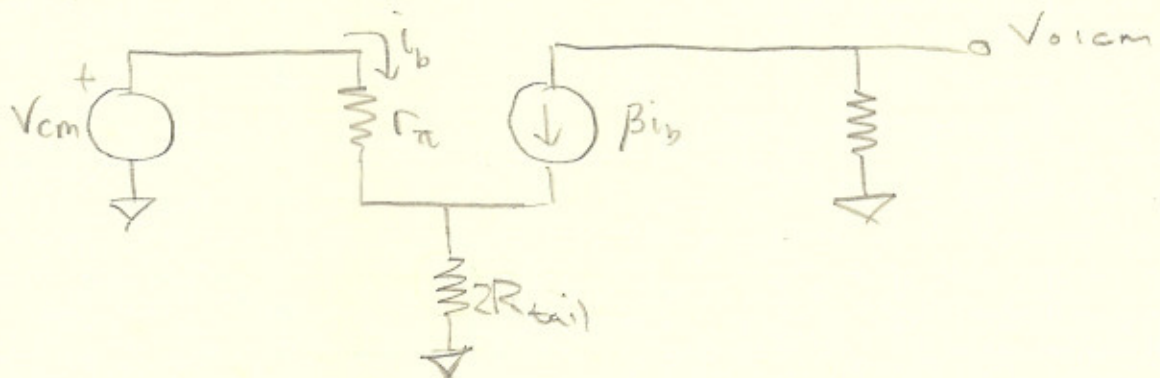

a_{cm} : common mode gain

$$a_{cm} = \frac{V_{o1cm}}{V_{cm}} = \frac{-g_m r_{\pi} R_c}{r_{\pi} + (1+\beta)2R_{tail}} = \frac{-\beta R_c}{r_{\pi} + (1+\beta)2R_{tail}}$$