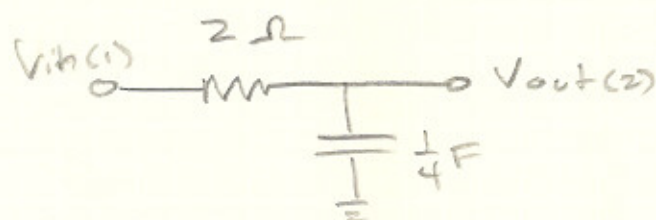


EX. Determine the TF of the circuit shown below.




use the transfer function to solve for

A.  $V_2(t)$ , when  $V_1(t)$  is a unit impulse function

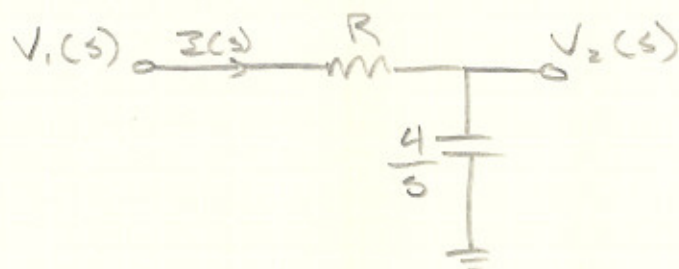B.  $V_2(t)$ , when  $V_1(t) = 5 \sin 2t$  (V)

SOL. A. Transform the above circuit to the s-domain.



$$G(s) = \frac{V_2(s)}{V_1(s)} = \frac{4/s}{2 + 4/s} = \frac{2}{s+2}$$

$$V_1(s) = 1$$

$$\therefore V_2(s) = \frac{2}{s+2} V_1(s)$$

$$V_2(t) = \mathcal{L}^{-1} \left[ \frac{2}{s+2} \right] = 2e^{-2t}$$

SOL. B.  $V_1(t) = 5 \sin 2t$

$$V_1(s) = \frac{5(2)}{s^2 + 4} = \frac{10}{s^2 + 4}$$

$$\begin{aligned}
 V_2(s) &= G(s)V_1(s) \\
 &= \frac{2}{s+2} \cdot \frac{10}{s^2+4} \\
 &= \frac{20}{(s+2)(s^2+4)}
 \end{aligned}$$

H/w, verify that

$$V_2(t) = \frac{5}{2}e^{-2t} - \frac{5}{2}\cos 2t + \frac{5}{2}\sin 2t$$

let

$$-\frac{5}{2}\cos 2t + \frac{5}{2}\sin 2t = E\sin(2t + \phi)$$

$$\left. \begin{aligned}
 -\frac{5}{2} &= E \sin \phi \\
 +\frac{5}{2} &= E \cos \phi
 \end{aligned} \right\} \begin{aligned}
 \tan \phi &= -1 \\
 \phi &= -45^\circ \\
 E &= \frac{\sqrt{2}5}{2}
 \end{aligned}$$

final answer

$$V_2(t) = \frac{5}{2}e^{-2t} + \frac{5\sqrt{2}}{2}\sin(2t - 45^\circ)$$

note: solve the same problem using phasors.

$$V_1 = (2 + \frac{1}{j\omega C})I, \quad I = j\omega C V_2$$

$$\therefore V_1 = \frac{2j\omega C + 1}{j\omega C} [j\omega C] V_2$$

$$V_1 = (2j\omega C + 1)V_2$$

which we can write as.

$$\frac{V_2}{V_1} = \frac{1}{2j\omega + 1} = \frac{1}{2(j)(\frac{1}{4})(2) + 1} = \frac{1}{j+1}$$

but  $v(t) = 5 \sin 2t \Rightarrow V_1 = 5 \angle 0^\circ$

$$\therefore V_2 = \frac{5 \angle 0^\circ}{1+j}$$

$$= \frac{5 \angle 0^\circ}{\sqrt{1^2+1^2} \angle 45^\circ}$$

$$= \frac{5}{\sqrt{2}} \angle -45^\circ$$

$$\therefore V_2 = \frac{5}{\sqrt{2}} \sin(2t - 45^\circ)$$

now here you should see that phasors are a subset from laplace transform. And will only give you the steady state.

LAPLACE TRANSFORM OF UNIT STEP FUNCTION.

$$u(t-a) = \begin{cases} 0 & t < a \\ 1 & t \geq a \end{cases}$$

Theorem:

$$\text{If } F(s) = \mathcal{L} f(t)$$

$$\text{and } f(t-a)u(t-a) = \begin{cases} 0, & t < a \\ f(t-a), & t \geq a \end{cases}$$

$$\mathcal{L} [f(t-a)u(t-a)] = e^{-as} F(s)$$

and vice versa.



## DEFINITIONS OF LINEAR SYSTEMS.

a system is said to be linear with respect to an excitation  $x(t)$  and a response  $y(t)$  if the following two properties are satisfied:

## PROPERTY 1 (amplitude property)

If the excitation  $x(t)$  produces a response  $y(t)$ , then the excitation  $Kx(t)$  should produce a response  $Ky(t)$ , where  $K$  is constant

EX. an input of 10V produces an output current of 2 A, then an input of 25V should produce a current of 5 A.

## PROPERTY 2 (super position principle)

If an excitation of  $x_1(t)$  produces a response of  $y_1(t)$  and an excitation of  $x_2(t)$  produces  $y_2(t)$  then:

an excitation of  $x_1(t) + x_2(t)$  should produce a response of  $y_1(t) + y_2(t)$

EX. 10 units produce an output of  $20t$  and an input of  $5\cos t$  produces  $10\sin t$  then

$10 + 5\cos t$  produces  $20 + 10\sin t$

## TRANSFER FUNCTIONS.

a general standard lumped system with an excitation  $x(t)$  and a response of  $y(t)$  can be described by an most general differential equation given by:

$$\textcircled{A} \quad b_m \frac{d^m y}{dt^m} + b_{m-1} \frac{d^{m-1} y}{dt^{m-1}} + \dots + b_0 y = a_n \frac{d^n x}{dt^n} + \dots + a_0 x$$

highest derivative in  $y$  determines the order

of the system. So the above equation describes an  $n^{\text{th}}$  order system. Further more, we will require  $n \geq n$

The next is to take the Laplace transform of both sides, then we will get a rather complicated terms with respect to the initial conditions

① Transformed will give:

$$[b_n s^n + b_{n-1} s^{n-1} + \dots + b_0] Y(s) + I_y = \dots + a_0 / s^n \\ = [a_n s^n + a_{n-1} s^{n-1} + \dots + a_0] X(s) + I_x$$

where  $I_x \neq I_y$  are the mass collection of initial conditions.

The last equation can be simplified to.

$$Y(s) = \left[ \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_0} \right] X(s) + \frac{I_x - I_y}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_0}$$

If the initial conditions are zero, then the equation becomes.

$$Y(s) = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_0} X(s)$$

or  $\frac{Y(s)}{X(s)} = G(s) = T.F.$


For convenience, write

$$N(s) = a_n s^n + a_{n-1} s^{n-1} + \dots + a_0$$


$$D(s) = b_n s^n + b_{n-1} s^{n-1} + \dots + b_0$$

then

$$G(s) = \frac{N(s)}{D(s)}$$

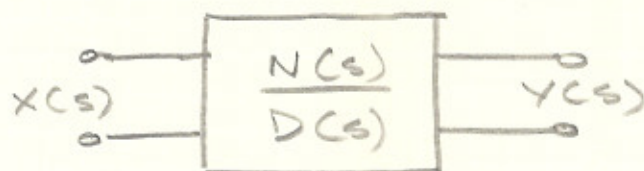


EX.

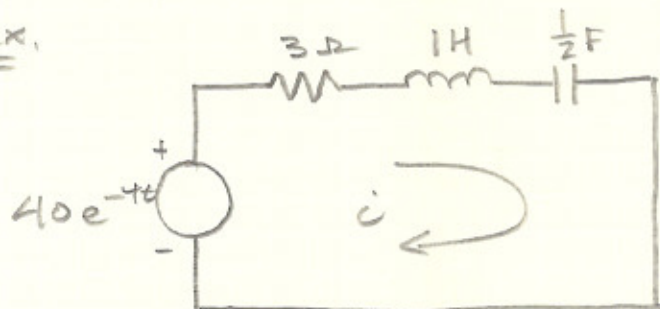

Assume that there is no initial energy stored in the circuit.

SOL The transformed circuit.

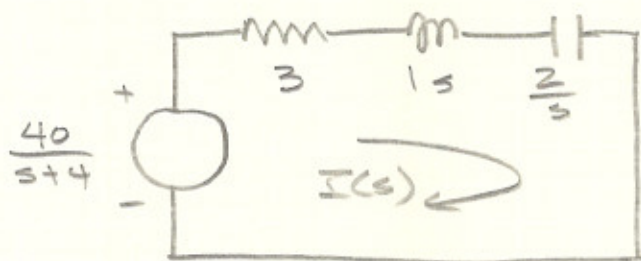

$$Z(s) = 3 + s + \frac{2}{s} = \frac{s^2 + 3s + 2}{s}$$

then we write

$$V(s) = Z(s) I(s)$$

$$\text{or } I(s) = \frac{V(s)}{Z(s)}$$

$$\text{T.F.} = \frac{1}{Z(s)} = Y(s)$$

$\swarrow$  admittance  
 $\nwarrow$  impedance

$$I(s) = \frac{s}{s^2 + 3s + 2} \left( \frac{40}{s+4} \right)$$



$$I(s) = \frac{40s}{(s^2+3s+2)(s+4)}$$

$$I(s) = \frac{40s}{(s+2)(s+1)(s+4)}$$

partial fractions, then

$$i(t) = \mathcal{L}^{-1} \left[ \frac{40}{s+2} + \frac{\left(-\frac{40}{3}\right)}{s+1} + \frac{\left(-\frac{80}{3}\right)}{s+4} \right]$$

$$i(t) = \left[ 40e^{-2t} - \frac{40}{3}e^{-t} - \frac{80}{3}e^{-4t} \right] u(t)$$


POLES, ZEROS, AND THEIR EFFECT ON NETWORK RESPONSE.

consider

$$G(s) = \frac{20(s+5)}{s(s+1)(s^2+6s+25)}$$


analysing

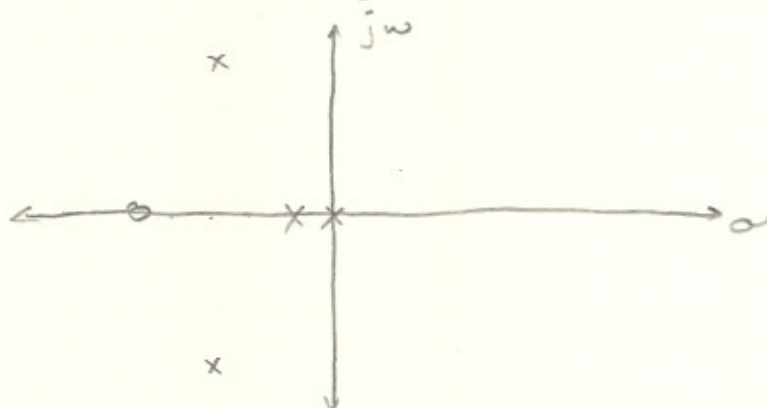- A.  $G(s)$  has a zero at  $-5$ , which will be represented by  $\circ$
- B.  $G(s)$  has poles at  $s=0$ ,  $s=-1$ , and  $s=-3 \pm j4$ .




# CASES (T, F.)

## 1. REAL ROOTS

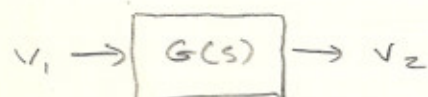

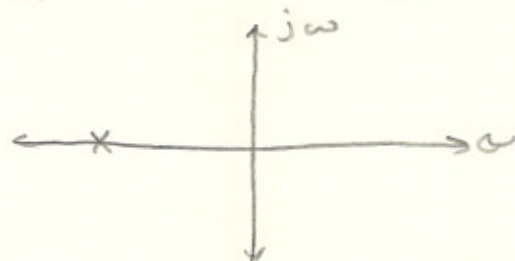
$$A. \frac{V_2(s)}{V_1(s)} = G(s) = \frac{1}{s+4}$$




if  $V_1(t)$  is a unit impulse function then  $V_1(s) = 1$

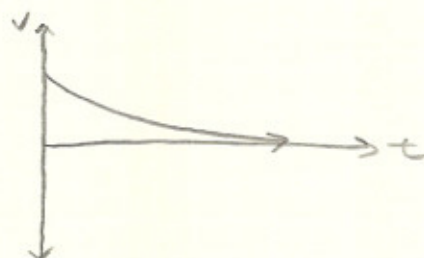
$$\therefore V_2(s) = \frac{1}{s+4} = e^{-4t}$$


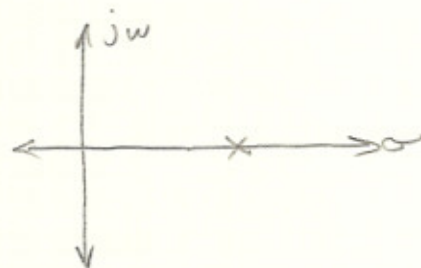
$$B. \frac{V_2(s)}{V_1(s)} = G(s) = \frac{1}{s-4}$$



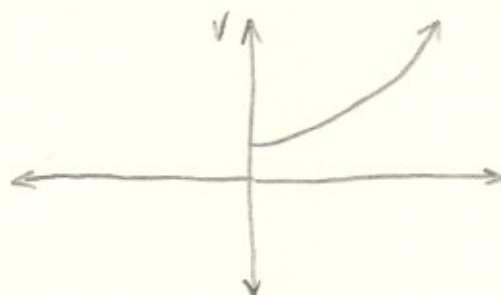when  $V_1(s) = 1$  then  $V_2(s) = \frac{1}{s-4}$   
and  $V_2(t) = e^{4t}$







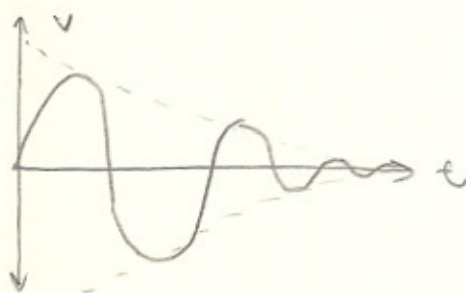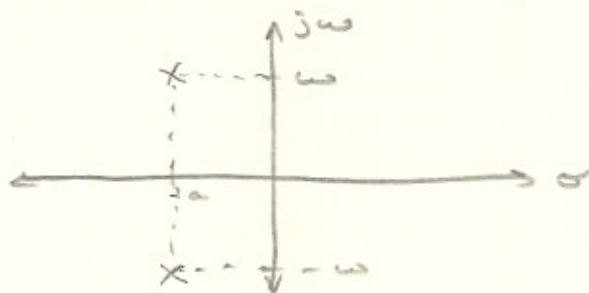
## 2. COMPLEX ROOTS

$$\frac{V_2(s)}{V_1(s)} = \frac{\omega}{(s+a)^2 + \omega^2} = G(s)$$

if  $V_1(s) = 1$  then  $V_2(t) = e^{-at} \sin \omega t$




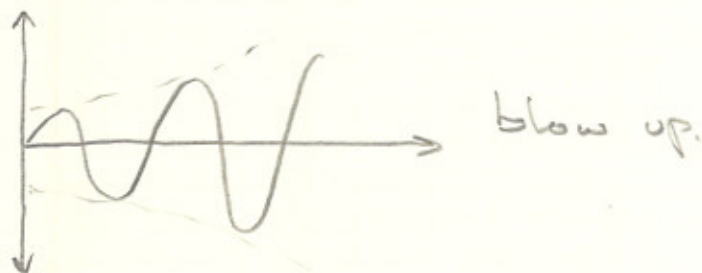if we had  $G(s) = \frac{\omega}{(s-a)^2 + \omega^2}$



## DOUBLE POLES.

$$\frac{V_2}{V_1} = \frac{1}{(s+a)^2}$$

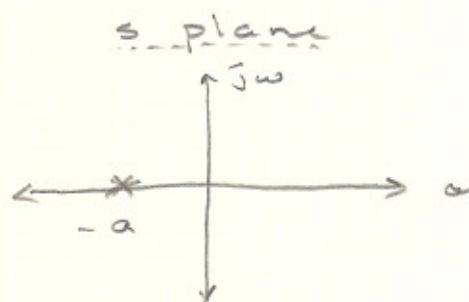


If  $V_1(s) = 1$

then  $\mathcal{L} V_2(s) = V_2(t) = te^{-at}$

- double conjugate poles
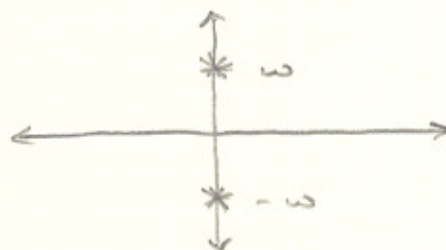
$$\frac{V_2}{V_1}(s) = \frac{s}{(s^2 + \omega^2)^2}$$




If  $V_1(s) = 1$

then  $V_2(t) = \frac{1}{2\omega} t \sin \omega t$

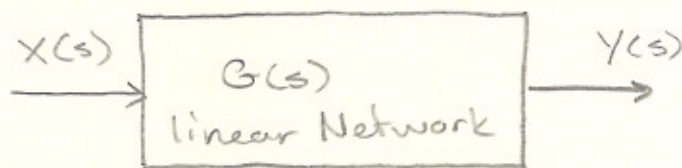
## STEADY STATE RESPONSE OF NETWORKS.

in general, a linear network can be represented by:



$$T.F. = G(s) = \frac{Y(s)}{X(s)}$$

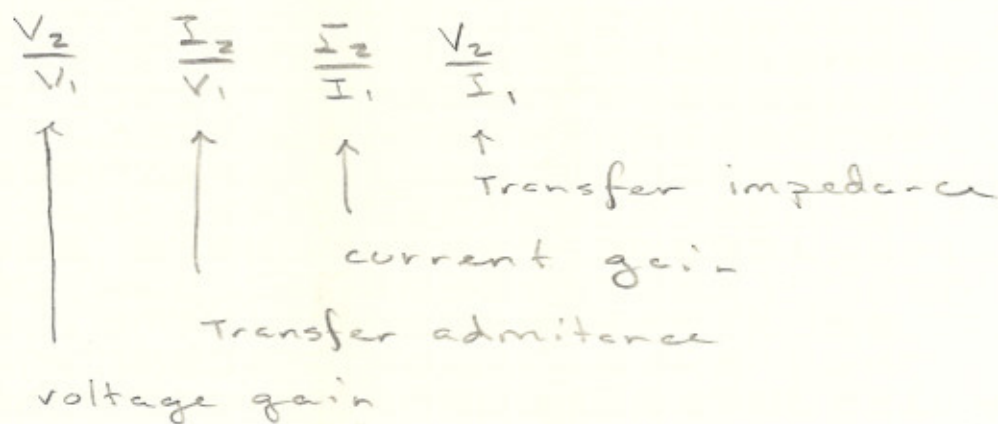if  $s$  is replaced by  $j\omega$ , a steady state response is obtained, assuming zero initial conditions, and since the input and output can either be voltages or currents, then we have 4 possible T.F.



Since  $G(j\omega)$  is a complex quantity, then we may write

$$G(j\omega) = |G(j\omega)| \angle \theta$$

which is a phasor, and since  $G(j\omega)$  is a complex quantity in general, then


$$G(j\omega) = \frac{N(j\omega)}{D(j\omega)}$$

- when  $N(j\omega)$  is equated to zero will give the zeros of the T.F.
- when  $D(j\omega)$  is equated to zero, it will give us the poles of the T.F.

Ex1

$$G(s) = \frac{Z}{s+2}$$

which comes from the following circuit.

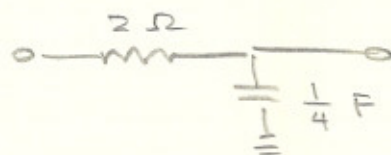



when the initial conditions are zero.

let  $s = j\omega$ , then the steady state TF. is given by:

$$G(j\omega) = \frac{2}{j\omega + 2} = \frac{2}{2 + j\omega}$$

we want to change this into

$$|G(j\omega)| \angle \beta$$

where

$|G(j\omega)| \rightarrow$  amplitude.

$\beta(\omega) \rightarrow$  phase angle.

therefore

$$|G(j\omega)| = \left| \frac{2}{2 + j\omega} \right| = \frac{2}{\sqrt{2^2 + \omega^2}}$$

$$\beta = -\tan^{-1}\left(\frac{\omega}{2}\right)$$

If  $v_i(t) = 5 \sin 2t$ , then  $v_i(t)$  can be written as a phasor

$$V_i(j\omega) = 5 \angle 0^\circ \quad \text{where } \omega = 2$$

then.

$$\begin{aligned} G(j2) &= \frac{2}{2 + j2} = \left| \frac{2}{2 + j2} \right| \angle \beta \\ &= \frac{1}{\sqrt{2}} \angle -45^\circ \end{aligned}$$

$$\begin{aligned}\therefore V_2(j\omega) &= G(j\omega) V_1(j\omega) \\ &= \left[ \frac{1}{\sqrt{2}} \angle 45^\circ \right] 5\end{aligned}$$

and the steady state response is phasor.

$$V_2(j\omega) = \frac{5}{\sqrt{2}} \angle 45^\circ$$

$$V_2(t) = \frac{5}{\sqrt{2}} \sin(2t - 45^\circ)$$

for linear circuits, the transform of interest are the ratios of polynomials in  $s$ , such functions are called rational functions

To find the inverse of laplace transform, we must find the waveforms corresponding to the rational function of the form.

$$F(s) = k \frac{(s-z_1)(s-z_2) \dots (s-z_m)}{(s-p_1)(s-p_2) \dots (s-p_n)}$$

$k$  is a scalar

$z_i$  are zeros

$p_i$  are poles

if  $n > m$ , there are more finite poles and then the infinite zeros and  $F(s)$  is called a proper rational function

If the denominator of  $F(s)$  has no repeated

roots, then  $F(s)$  is said to have simple poles

If proper rational function has only simple poles, then it can be decomposed into

$$F(s) = \frac{k_1}{(s-p_1)} + \frac{k_2}{(s-p_2)} + \dots + \frac{k_n}{(s-p_n)}$$

$$\mathcal{L}^{-1}(F(s)) = k_1 e^{-p_1 t} + k_2 e^{-p_2 t} + \dots + k_n e^{-p_n t}$$

$k_1, k_2, \dots, k_n$  are known as residues.  
recall the cover up method.

$$k_i = \left[ (s-p_i) F(s) \right]_{s=p_i}$$

### REGARDING COMPLEX POLES

we may extend the above for complex roots, consider the following:

$$F(s) = \underbrace{\dots}_{\text{real poles}} + \frac{\bar{K}}{(s+\alpha-j\beta)} + \frac{K^*}{(s+\alpha+j\beta)}$$

The residues  $\bar{K}$  &  $K^*$  at the conjugate poles are themselves conjugates b/c  $F(s)$  is  $\frac{\bar{K}}{\bar{K}}$

$$\text{then } \bar{K} = |\bar{K}| e^{j\theta} \quad \& \quad K^* = |\bar{K}| e^{-j\theta}$$

then the waveforms corresponding to the above 2 terms are ...

$$f(t) = \underbrace{\dots}_{\text{real part}} + |\bar{K}| e^{j\theta} e^{(-\alpha+j\beta)t} + |\bar{K}| e^{-j\theta} e^{(-\alpha-j\beta)t}$$



rearranging we get.

$$f(t) = \dots + 2|K|e^{-\alpha t} \left[ \frac{e^{j(\beta t + \theta)} + e^{-j(\beta t + \theta)}}{2} \right]$$

or

$$f(t) = \dots + 2|K|e^{-\alpha t} \cos(\beta t + \theta)$$

for h/w try to find  $\mathcal{L}^{-1}$

$$F(s) = \frac{20(s+3)}{(s+1)(s^2+2s+5)}$$

## COMPLEX NUMBERS

complex numbers were invented to permit the extraction of roots of negative numbers.

## NOTATION

$$j = \sqrt{-1}$$

$$\bar{z} = a + jb \quad (\text{rectangular form})$$

$$\bar{z} = |\bar{z}| e^{j\theta} = |\bar{z}| \angle \theta \quad (\text{polar form})$$


$$|\bar{z}| = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1}\left(\frac{b}{a}\right)$$

we may write

$$|\bar{z}| \cos \theta = a$$

$$|\bar{z}| \sin \theta = b$$

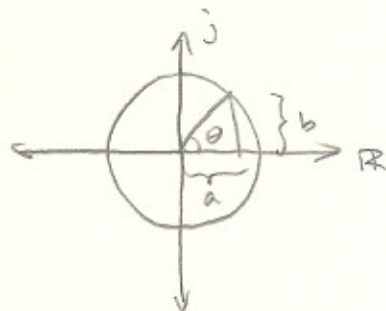

or

$$|\bar{z}| e^{j\theta} = |\bar{z}| (\cos \theta + j \sin \theta)$$

Ex:

$$\bar{z} = 3 + j4 = 5 e^{j53.1^\circ} = 5 \angle 53.1^\circ$$

Ex:

$$\bar{z} = -4 + j2 = 4.472 e^{j173.4^\circ} = 4.472 \angle 173.4^\circ$$

DIVISION.

$$\frac{\bar{z}_1}{\bar{z}_2} = \frac{|\bar{z}_1|}{|\bar{z}_2|} e^{j(\theta_1 - \theta_2)}$$

ADDITION

$$\bar{z}_1 + \bar{z}_2 = a_1 + jb_1 + a_2 + jb_2 = (a_1 + a_2) + j(b_1 + b_2)$$

MULTIPLICATION OF CONJUGATES

$$\bar{z} \cdot \bar{z}^* = a^2 + b^2 = |\bar{z}|^2$$

Ex:

$$F(s) = \frac{20(s+3)}{(s+1)(s^2+2s+5)}$$

Sol:  $F(s)$  has a simple pole at  $s=-1$  and a pair of complex conjugate poles which are given by

$$(s^2+2s+5) = (s+1-j2)(s+1+j2)$$

partial fractions of  $F(s)$

$$F(s) = \frac{k_1}{s+1} + \frac{\bar{k}_2}{s+1-j2} + \frac{\bar{k}_2^*}{s+1+j2}$$

using coverup algorithm, then.

$$k_1 = \frac{20(s+3)}{s^2+2s+5} \Big|_{s=-1} = 10$$

$$\bar{k}_2 = \frac{20(s+3)}{(s+1)(s+1+j2)} \Big|_{s=-1+j2} = -5-j5 = 5\sqrt{2} e^{j\frac{3\pi}{4}}$$



$$\overline{k_2}^* = -5 + j5 = 5\sqrt{2} e^{j\frac{3}{4}\pi}$$

$$F(s) = \frac{10}{s+1} + \frac{5\sqrt{2} e^{j\frac{3}{4}\pi}}{s+1-j2} + \frac{5\sqrt{2} e^{-j\frac{3}{4}\pi}}{s+1+j2}$$

$$f(t) = \left\{ 10e^t + 10\sqrt{2} e^{-t} \cos\left(2t + \frac{3}{4}\pi\right) \right\} u(t)$$

note:

$$\frac{\overline{k}}{s+\alpha-j\beta} + \frac{\overline{k}^*}{s+\alpha+j\beta} = F(s)$$

$$\mathcal{L}^{-1}[F(s)] = z|\overline{k}|e^{-\alpha t} \cos(\beta t + \theta)$$

$$\frac{\overline{k}}{(s+\alpha-j\beta)^2} + \frac{\overline{k}^*}{(s+\alpha+j\beta)^2} = F(s)$$

$$\mathcal{L}^{-1}[F(s)] = zt|\overline{k}|e^{-\alpha t} \cos(\beta t + \theta)$$

where  $\overline{k} = |\overline{k}|e^{j\theta}$   
 $\overline{k}^* = |\overline{k}|e^{-j\theta}$

## MULTIPLE POLES

consider

$$F(s) = \frac{k(s-z_1)}{(s-p_1)(s-p_2)^2}$$

it has a multiple pole at  $s=p_1$  and  $s=p_2$ 

$$F(s) = \frac{1}{s-p_2} \left( \frac{k(s-z_1)}{(s-p_1)(s-p_2)} \right)$$

and

$$F(s) = \frac{1}{s-p_2} \left[ \frac{C_1}{s-p_1} + \frac{k_{22}}{s-p_2} \right]$$

then

$$F(s) = \frac{C_1}{(s-p_1)(s-p_2)} + \frac{k_{22}}{(s-p_2)^2}$$

Expanding.

$$\frac{C_1}{(s-p_1)(s-p_2)} = \frac{k_1}{s-p_1} + \frac{k_{21}}{s-p_2}$$

 $\therefore$ 

$$F(s) = \frac{k_1}{s-p_1} + \frac{k_{21}}{s-p_2} + \frac{k_{22}}{(s-p_2)^2}$$

$$\mathcal{L}^{-1}[F(s)] = \{k_1 e^{p_1 t} + k_{21} e^{p_2 t} + k_{22} t e^{p_2 t}\} u(t)$$

Ex: find the inverse.

$$F(s) = \frac{4(s+3)}{s(s+2)^2}$$

$$F(s) = \frac{1}{(s+2)} \underbrace{\left[ \frac{4(s+3)}{s(s+2)} \right]}_{F_0(s)}$$

$$F_0(s) = \frac{4(s+3)}{s(s+2)} = \frac{A_1}{s} + \frac{A_2}{s+2}$$

cover up technique

$$A_1 = \frac{4s(s+3)}{s(s+2)} \bigg|_{s=0} = 6$$

$$A_2 = \frac{(s+2)4(s+3)}{s(s+2)} \bigg|_{s=-2} = -2$$

$\therefore$

$$F(s) = \frac{1}{s+2} \left[ \frac{6}{s} - \frac{2}{s+2} \right]$$

$$F(s) = \frac{6}{s(s+2)} - \frac{2}{(s+2)^2}$$

expand.

$$F(s) = \frac{3}{s} - \frac{3}{s+2} - \frac{2}{(s+2)^2}$$

$$\mathcal{L}^{-1}[F(s)] = \{3 - 3e^{-2t} - 2te^{-2t}\} u(t)$$