

## LC FOSTER NETWORKS

1. foster network 1 - partial fraction  $Z(s)$
2. foster network 2 - partial fraction  $Y(s)$

FOSTER 1

general expression for  $Z(s)$  given by:

$$\frac{Z(s) = k(s^2 + \omega_{z_1}^2)(s^2 + \omega_{z_2}^2) \dots (s^2 + \omega_{z_n}^2)}{s(s^2 + \omega_{p_1}^2)(s^2 + \omega_{p_2}^2) \dots (s^2 + \omega_{p_n}^2)}$$

If the degree of  $N$  is higher than the degree of  $D$ , then we may perform division and we may write:

$$Z(s) = ks + Z_1(s)$$

Expand  $Z_1(s)$  by partial fractions and combining complex conjugate pairs, we get:

$$Z(s) = ks + \frac{k_0}{s} + \frac{k_1 s}{(s^2 + \omega_{p_1}^2)} + \dots + \frac{k_n s}{(s^2 + \omega_{p_n}^2)}$$

by combining complex conjugate terms, we mean:

$$\frac{\bar{k}_{pi}}{(s - j\omega_{pi})} + \frac{\bar{k}_{pi}^*}{(s + j\omega_{pi})} = \frac{(k_{pi} + \bar{k}_{pi}^*)s + j\omega_{pi}(k_{pi} - \bar{k}_{pi}^*)}{(s^2 + \omega_{npi}^2)}$$

$$= \frac{2k_{pi}s}{(s^2 + \omega_{pi}^2)}, \text{ let } k_i = 2k_{pi} = \frac{k_i s}{(s^2 + \omega_{npi}^2)}$$

$$Z(s) = ks + \frac{k_0}{s} + \frac{k_1 s}{(s^2 + \omega_{p1}^2)} + \dots + \frac{k_n s}{(s^2 + \omega_{pn}^2)}$$

where all k's are positive and can be evaluated using the cover up technique.

$$k_0 = s Z(s) \Big|_{s=0}$$

$$k_i = \frac{(s^2 + \omega_{pi}^2)}{s} Z(s) \Big|_{s^2 = -\omega_{pi}^2}, \quad i \in \mathbb{I}$$

Ex: Obtain the Foster I realization given by

$$Z(s) = \frac{s(s^2 + 4)}{(s^2 + 1)(s^2 + 9)}$$

$$k = 0$$

$$k_0 = 0$$

$$Z(s) = \frac{k_1 s}{(s^2 + 1)} + \frac{k_2 s}{(s^2 + 9)}$$

$$k_1 = Z(s) \frac{(s^2 + 1)}{s} \Big|_{s^2 = -1} = \frac{s^2 + 4}{s^2 + 9} \Big|_{s^2 = -1} = \frac{3}{8}$$

$$k_2 = Z(s) \frac{(s^2 + 9)}{s} \Big|_{s^2 = -9} = \frac{s^2 + 4}{s^2 + 1} \Big|_{s^2 = -9} = \frac{5}{8}$$

$$Z(s) = Z_1(s) + Z_2(s) = \frac{\frac{3}{8}s}{s^2 + 1} + \frac{\frac{5}{8}s}{s^2 + 9}$$

$$Z_1(s) = \frac{1}{sL} \left[ \frac{1}{sC} + 1 \right]$$

$$\frac{1}{Z_1} = sC + \frac{1}{sL} = \frac{s^2 + LC + 1}{sL}$$

$$Z_1 = \frac{sL}{s^2 L C + 1} \quad \text{compared to} \quad \frac{\frac{3}{8}s}{s^2 + 1}$$

$$\therefore L = \frac{3}{8} \quad LC = 1$$

$$\therefore C = \frac{8}{3}$$

$$Z_2(s) = \frac{1}{sL} \left[ \frac{1}{sC} + 1 \right]$$

$$Z_2 = \frac{sL}{s^2 LC + 1} \quad \text{compared to} \quad \frac{\frac{5}{8}s}{s^2 + 9}$$

$$L_2 = \frac{5}{72}, \quad C_2 = \frac{100}{5}$$

## FOSTER II NETWORK.

here we expand  $Y(s)$  by partial fractions.  
In most general form..

$$Y(s) = \frac{k(s^2 + \omega_{z_1}^2)(s^2 + \omega_{z_2}^2) \dots (s^2 + \omega_{z_{n+1}}^2)}{s(s^2 + \omega_{p_1}^2)(s^2 + \omega_{p_2}^2) \dots (s^2 + \omega_{p_n}^2)}$$

which has a partial fraction expansion given by,

$$Y(s) = ks + \frac{k_0}{s} + \frac{k_1 s}{(s^2 + \omega_{p_1}^2)} + \dots + \frac{k_n s}{(s^2 + \omega_{p_n}^2)}$$

All  $k$ 's are positive real values, and can be found as follows,

$$k_0 = s Y(s) \Big|_{s=0}$$

$$k_i = \left. \frac{(s^2 + \omega_{p_i}^2)}{s} Y(s) \right|_{s^2 = \omega_{p_i}^2}, i \in I$$

$Y(s)$  represents the sum of admittances, hence network realization contains structures in parallel.


The first term is  $ks$ , which is the admittance of a capacitor. The second term  $\frac{k_0}{s}$  is the admittance of an inductor.

The third(etc) terms, are of the form

$$Y = \frac{k_i s}{(s^2 + \omega_{p_i}^2)} = \frac{1}{s(\frac{1}{k_i}) + \frac{1}{s(\frac{k_i}{\omega_{p_i}^2})}} = \frac{1}{z}$$

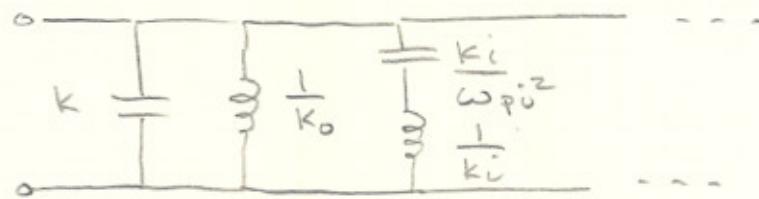2.

Based on the above results, the complete realization is shown below.



EX: obtain the Foster II realization for

$$Z(s) = \frac{s(s^2+4)}{(s^2+1)(s^2+9)}$$

$$Y(s) = \frac{(s^2+1)(s^2+9)}{s(s^2+4)}$$

$$= ks + \frac{k_0}{s} + \frac{k_1 s}{s^2+4}$$

$$k = 1$$

$$k_0 = \left. \frac{(s^2+1)(s^2+9)}{(s^2+4)} \right|_{s=0} = \frac{9}{4} \Omega^{-1}$$

$$k_1 = \left. \frac{(s^2+1)(s^2+9)}{s^2} \right|_{s^2=-4} = \frac{15}{4}$$

$$Y = Y_1 + Y_2 + Y_3$$

$$Y_1 = s ; Y_2 = \frac{9}{4}s = \frac{4}{9} H$$

$$Y_3 = \frac{4}{15} H \approx \frac{15}{16} H$$

## RC FOSTER AND CAUER NETWORKS.

### FOSTER I

$$Z(s) = \frac{k \left\{ (s + \alpha_2)(s + \alpha_4) \dots \right\}}{\left\{ (s + \alpha_1)(s + \alpha_3) \dots \right\}}$$

$k$  is positive.


$$0 \leq \alpha_1 < \alpha_2 < \alpha_3 < \alpha_4 \dots$$

partial fractions give

$$Z(s) = k + \frac{k_1}{s} + \frac{k_3}{s + \alpha_3} + \frac{k_5}{s + \alpha_5}$$

$k$ 's are evaluated using coverup technique.

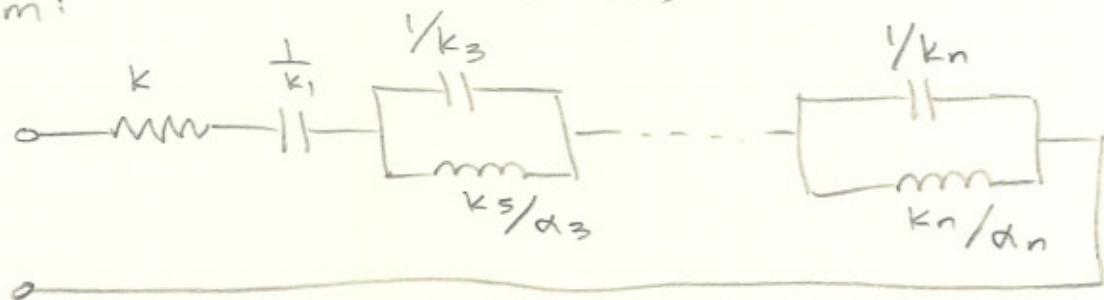all  $k$ 's are positive and real,  $\therefore$  RC foster I networks realization of  $Z(s)$  will have the form:



### FOSTER II

start with  $Z(s)$  which is given by

$$Z(s) = \frac{k(s + \alpha_2)(s + \alpha_4) \dots}{(s + \alpha_1)(s + \alpha_3) \dots}$$

If  $\alpha_1 = 0$  hence  $k = \frac{1}{K}$


$$Y(s) = \frac{ks(s + \alpha_3)(s + \alpha_5)}{(s + \alpha_2)(s + \alpha_4)} \dots$$

$$\frac{Y(s)}{s} = \frac{k(s + \alpha_3)(s + \alpha_5)}{(s + \alpha_2)(s + \alpha_4)} \dots$$

partial fractions.

$$\frac{Y(s)}{s} = k + \frac{k_2}{(s + \alpha_2)} + \frac{k_4}{(s + \alpha_4)} + \dots + \frac{k_n}{(s + \alpha_n)}$$

foster II realization.

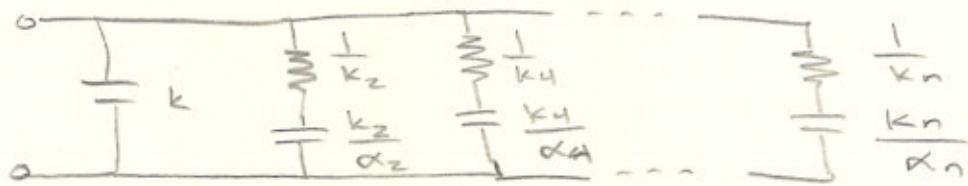

Ex: given

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$$

realize foster I & II networks, and also  
realize Cauer I & II

## 2<sup>nd</sup> ORDER SYSTEMS

most general 2<sup>nd</sup> order functions are known as the biquad functions as shown below.

$$T(s) = \frac{C_2 s^2 + C_1 s + C_0}{D_2 s^2 + D_1 s + D_0}$$

$$T(s) = \frac{\frac{C_2}{D_2} s^2 + \frac{C_1}{D_2} s + \frac{C_0}{D_2}}{s^2 + \frac{D_1}{D_2} s + \frac{D_0}{D_2}}$$

and we write

$$T(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0}$$

$$T(s) = \frac{N(s)}{D(s)}$$

when poles are properly placed  $N(s)$  can be adjusted to make

$T(s)$  low pass ( $a_2 = a_1 = 0$ )

$T(s)$  band pass ( $a_2 = a_0 = 0$ )

$T(s)$  high pass ( $a_1 = a_0 = 0$ )

$T(s)$  all pass ( $a_2 = 1, a_1 = -b_1, a_0 = b_0$ )

$T(s)$  band stop ( $a_1 = 0$ )

The above designations refer to  $|T(s)| = |T(j\omega)|$   
= magnitude of transfer function

The above designations of  $|T(\omega_j)|$  indicate how the amplitude of sine waves with different freq are affected in the steady state as they are processed by the network.

For example, low pass function passes low pass function passes low freq and rejects high freq.



$$\text{let: } D(s) = (s + \alpha)^2 + \beta^2 \\ = s^2 + 2\alpha s + \alpha^2 + \beta^2$$

$$\text{let } \omega_0^2 = \alpha^2 + \beta^2$$

$$\text{let } 2\alpha = \frac{\omega_0}{Q}$$

$$\therefore D(s) = s^2 + \frac{\omega_0}{Q} s + \omega_0^2$$

where

$$\omega_0 = \sqrt{\alpha^2 + \beta^2}$$

$$Q = \frac{\sqrt{\alpha^2 + \beta^2}}{2\alpha}$$

If  $\omega_0$  and  $Q$  are given, we can find  $\alpha$  and  $\beta$  from:

$$\alpha = \frac{\omega_0}{2Q}$$

$$\beta = \omega_0 \sqrt{1 - \frac{1}{4Q^2}}$$

from  $D(s) = (s + \alpha)^2 + \beta^2$


if we evaluate  $D(s) = 0$

$$(s + \alpha)^2 + \beta^2 = 0$$

$$s^2 + 2\alpha s + \alpha^2 + \beta^2 = 0$$

$$s = \frac{-2\alpha \pm \sqrt{(2\alpha)^2 - 4(\alpha^2 + \beta^2)}}{2}$$

$$s = -\alpha \pm j\beta$$

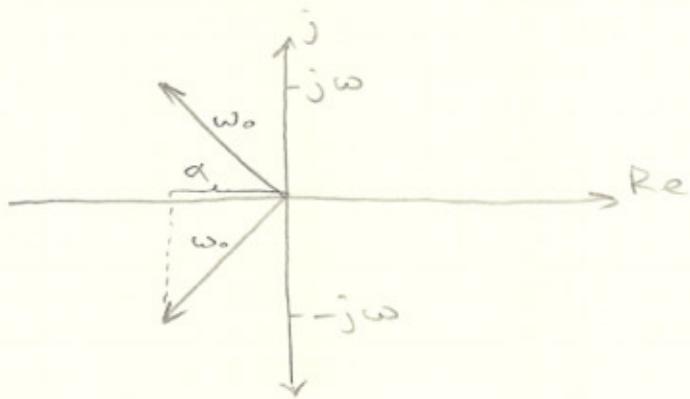

$\omega_0$ : is the magnitude of the poles, distance from the origin to the poles.

$\alpha$ : is the measure of the slope of the radial line from the origin to the pole. The higher the  $\alpha$  the steeper the radial lines.

when  $\alpha \leq \frac{\pi}{2}$ , roots are real. Let us check this out.


$$D(s) = s^2 + \frac{\omega_0}{\alpha} s + \omega_0^2$$

$$s = \frac{-\omega_0/\alpha \pm \sqrt{(\omega_0/\alpha)^2 - 4\omega_0^2}}{2}$$

$$s = \frac{\omega_0/(1/2) \pm \sqrt{(\omega_0/(1/2))^2 - 4\omega_0^2}}{2}$$

$$= -\frac{2\omega_0}{2} = -\omega_0$$

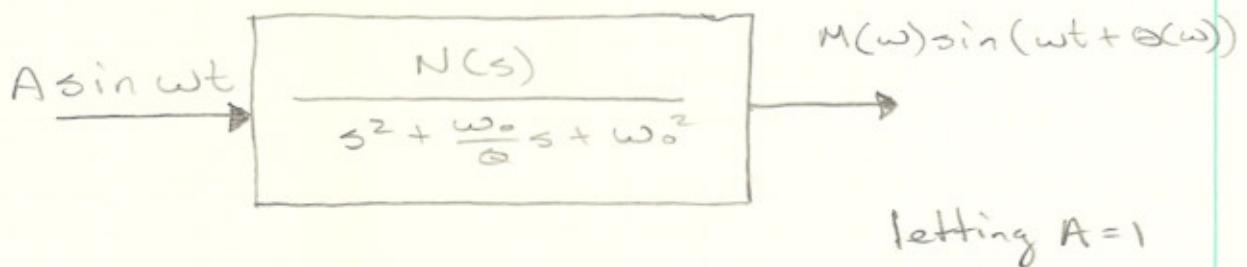Consider a sinusoidal steady state response given below.




letting  $A=1$

The above is represented by:

$$\frac{M(\omega)}{A} = |T(j\omega)| = \left| \frac{N(s)}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \right|$$

remember that  $s=j\omega$

$$M(\omega) = \frac{|N(j\omega)|}{\sqrt{[\omega_0^2 - \omega^2]^2 + (\frac{\omega_0 \omega}{Q})^2}}$$

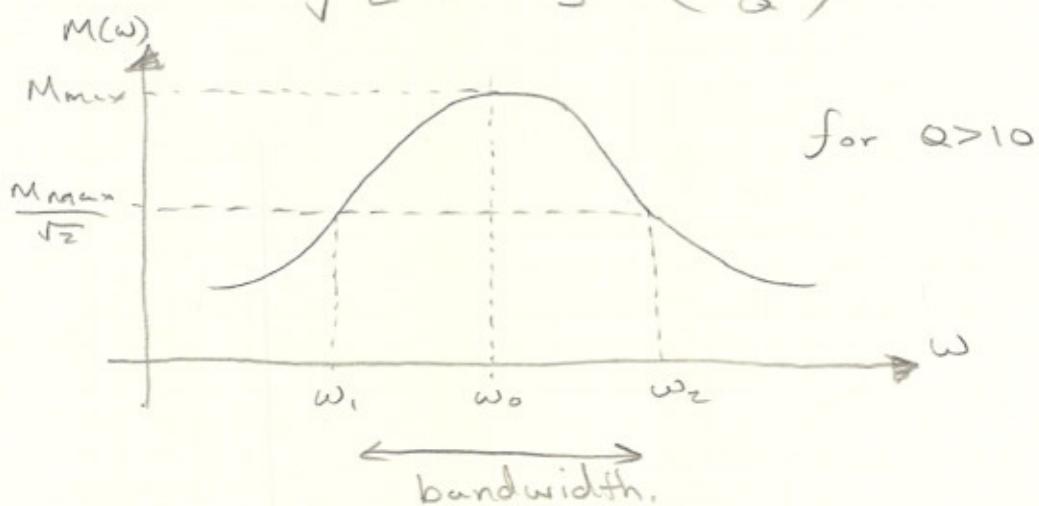

note: for steady state response.

Note: for all practical purposes  $M(\omega)$  versus  $\omega$  peaks at  $\omega = \omega_0$ .

The two freq at either side of  $\omega_0$ , where the magnitudes

$$M(\omega) = \frac{[M(\omega)]_{\max}}{\sqrt{2}}$$

this is also referred to as the 3dB frequencies.

## DECIBELS

Is the logarithmic measurement of the ratio of one power to another or one voltage to another.

$$\text{dB} = 10 \log \left( \frac{P_{\text{out}}}{P_{\text{in}}} \right)$$

$$\text{dB} = 20 \log \left( \frac{V_{\text{out}}}{V_{\text{in}}} \right)$$

$$V_{\text{out}} = \frac{V_{\text{in}}}{\sqrt{2}} = 0.707 V_{\text{in}}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = 0.707$$

$$\therefore 20 \log(0.707) = -3 \text{ dB.}$$

Q

the higher the value of Q, the narrower the bandwidth, since

$$\text{BW} = \frac{\omega_0}{Q},$$

and the more selective the system is for sinusoidal signals. High Q indicates that the poles are closer to the imaginary axis

## SUMMARY (biquad functions)

$$TF = k \left\{ \frac{\alpha_2 s^2 + \alpha_1 \frac{\omega_0}{Q} s + \alpha_0 \omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} \right\}$$

the above is the most common biquad functions used in a variety of filter designs.

$k$  = d.c. gain.

$\alpha_2, \alpha_1$ , and  $\alpha_0$  are constants in we  
let  $s = j\omega$

let  $k=1$

$$T(j\omega) = \frac{(\alpha_0 \omega_0^2 - \alpha_2 \omega^2) + j \alpha_1 \left( \frac{\omega_0}{Q} \right) \omega}{(\omega_0^2 - \omega^2) + j \left( \frac{\omega_0}{Q} \right) \omega}$$

let  $\omega = \underline{2\pi f}$

It can be shown that:

$$Q = \frac{\omega_0}{BW} = \frac{\omega_0}{\omega_2 - \omega_1}$$

$\omega_2$ : high cut off freq.

$\omega_1$ : low cut off freq.

different values for  $a_2, a_1, a_0$  yield to

Filter	$a_2$	$a_1$	$a_0$	TF.
LP	0	0	1	$\frac{k\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$
HP	1	0	0	$\frac{ks^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$
BP	0	1	0	$\frac{k(\frac{\omega_0}{Q})s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$
Bandreject	1	0	1	$\frac{k(s^2 + \omega_0^2)}{s^2 + (\frac{\omega_0}{Q})s + \omega_0^2}$
All Pass	1	-1	1	$\frac{k(s^2 - \frac{\omega_0}{Q}s + \omega_0^2)}{s^2 + (\frac{\omega_0}{Q})s + \omega_0^2}$

## ROOT LOCI AND SENSITIVITY FUNCTIONS. 2<sup>ND</sup> ORDER.

a system transfer function for


$$T(s) = \frac{V_o}{V_i}(s)$$

relates the output to the input variable.

physical electrical systems, in general depart from desired system characteristics for many reasons, for example, Capacitor and resistors are not constants, and their values change with temp, age, etc; and the above include inductors. In practical circuits, capacitor & resistor values change by as much as  $\pm 5\%$  from their exact values.

So in real life a system which is designed with a certain pole-zero distribution to achieve a specified freq response may exhibit different characteristics when built and tested. So it is important to consider the impact of changes in component response.

Consider the following:

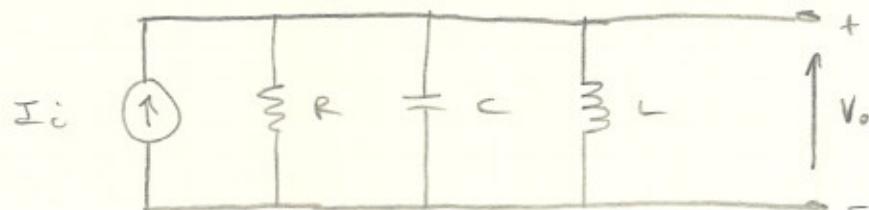

$$TF = \left( \frac{V_o}{I_i} \right) (s) = \frac{s}{\frac{1}{C} \left\{ s^2 + \frac{1}{RC}s + \frac{1}{LC} \right\}}$$

$$\text{here, } \omega_0 = \frac{1}{\sqrt{LC}}, \quad Q = R \sqrt{\frac{C}{L}}$$

Comparing to earlier work, we see that


$$\alpha = \frac{1}{2RC}$$

$$\beta = \sqrt{\frac{1}{LC} - \left( \frac{1}{2RC} \right)^2}$$

from the above we notice that  $\omega_0$  depends on  $L$  and  $C$  and not of  $R$

$\alpha$  is independant of  $L$ , so we can vary  $\alpha$  of the pole and keep  $\omega_0$  constant by changing by changing  $R$ .

consider the following circuit

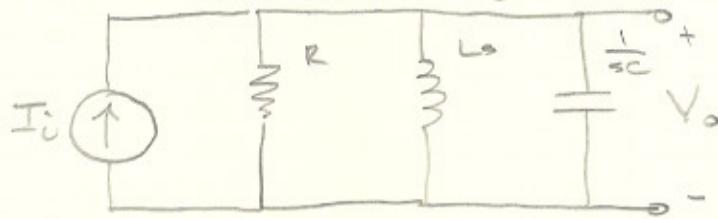

$$TF = \frac{V_o}{I_i} = \frac{s/C}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

$\therefore$  poles are

$$s = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}}{2}$$

$$s = \frac{-\frac{1}{2RC} \pm \frac{1}{2}\sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}}{2}$$

case 1

$$\left(\frac{1}{RC}\right)^2 = \frac{4}{LC} \Rightarrow C = \frac{L}{4R^2}$$

hence

$$s = \frac{-\frac{1}{2RC}}{\frac{1}{2RC}} = -\frac{2R}{L}$$

$$C = \frac{L}{4R^2} \Rightarrow s = -\frac{2R}{L}$$

case 2:

$$D(s) = s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 \quad \text{given roots}$$

$$s^2 LR + s \frac{L}{C} + \frac{R}{C} = 0$$

when  $C \rightarrow \infty, s^2 \rightarrow 0$

when  $C \rightarrow 0, s \rightarrow -\frac{R}{L}$

case 3:  $\left(\frac{1}{RC}\right)^2 > \frac{4}{LC}$

$$s = \frac{-1}{2RC} \pm \frac{1}{2} \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}$$

results in a real number.


hence we have poles on the real axis.

case 4

$$\left(\frac{1}{RC}\right)^2 < \frac{4}{LC}$$

$$s = \frac{-1}{2RC} + \frac{1}{2} j \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}$$
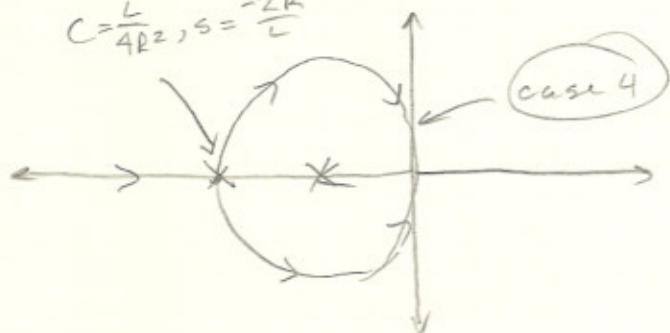
$$C = \frac{L}{4R^2}, s = \frac{-2R}{L}$$



## SENSITIVITY

The response of a practical network is likely to deviate from that predicted by theory. This is due to the component tolerances and quite often operational amp. Aging may also play a role.

It is important then to show how the network is sensitive to component variations. For example, a filter designer may want to know the extent to which a 1% variation in a given resistance or capacitance may effect  $\omega_0$  and BW.

Given a filter parameter  $y$  such as  $\omega_0$  and  $Q$ , a given filter component  $x$  such as resistance  $R$  or capacitance  $C$ , the sensitivity function is defined as:

$$S_x^y = \frac{\partial y/y}{\partial x/x} = \frac{x}{y} \frac{\partial y}{\partial x}$$

the partial derivatives are used, since the filter parameter depends on more than just one component.

The sensitivity function satisfies the following useful properties.

$$S_{\frac{1}{x}}^y = S_x^{y/x} = -S_x^y \quad \textcircled{A}$$

$$S_x^{y_1 y_2} = S_x^{y_1} + S_x^{y_2} \quad \textcircled{B}$$


$$S_x^{y_1/y_2} = S_x^{y_1} - S_x^{y_2} \quad \textcircled{C}$$

$$S_x^{x^n} = n \quad \textcircled{D}$$

$$S_{x_1}^y = S_{x_2}^y S_{x_1}^{x_2} \quad \textcircled{E}$$
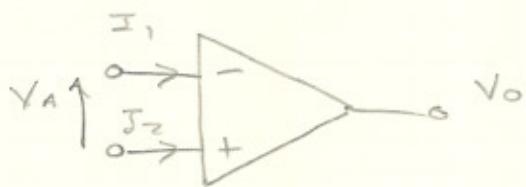
## THE OP AMP.

An ideal op amp will have a very high gain and the symbol of the op amp is shown below.




Ideal op amp

1.  $\infty$  input impedance.

2.  $I_1 = I_2 = 0$

3.  $0$  output impedance.  $V_o$  is independent of current drawn.

## NON INVERTING AMP

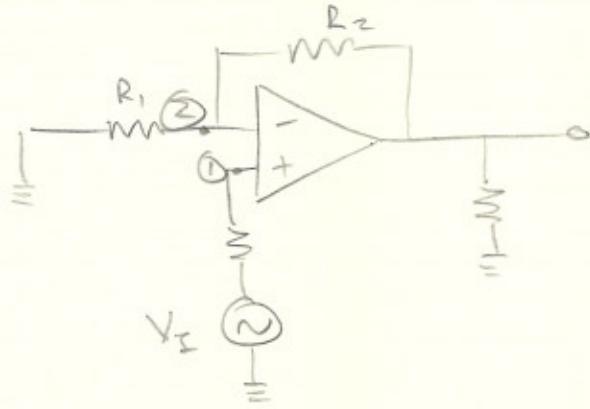


$$V_0 = V_2$$

$$\frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$$

$$\frac{V_o(s)}{V_i(s)} = 1 + \frac{Z_2(s)}{Z_1(s)}$$

## INVERTING AMP.

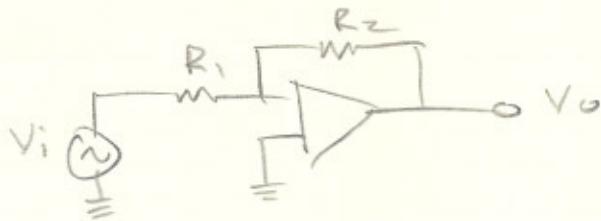

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$

# DIFFERENCE AMP

