

$$V - \frac{V - V_{in} - V_T}{R + R_D + R_i} \cdot R \leq V_{out}^0$$

$$\frac{V(R + R_D + R_i) - (V - V_{in} - V_T)R}{R + R_D + R_i} \leq V_{out}^0$$

$$\frac{VR + V(R_D + R_i) - VR + (V_{in} - V_T)R}{R + R_D + R_i} \leq V_{out}^0$$

$$V(R_D + R_i) - R(V_{in} - V_T) \leq V_{out}^0 R + V_{out}^0 (R_D + R_i)$$

$$-R(V_{in} - V_T - V_{out}^0) \leq V_{out}^0 (R_D + R_i) - V(R_D + R_i)$$

$$R \geq \frac{(V_{out} - V)(R_D + R_i)}{V_{in} - V_T - V_{out}^0}$$

$$V_{out} \geq V_{out}^1$$

$$I = \frac{V}{R + R_D}$$

$$V_{out} = R_D I$$

$$V_{out} = \frac{R_L}{R + R_L} V \geq V_{out}'$$

$$R_L V \geq V_{out}' (R + R_L)$$


$$R_L (V - V_{out}') \geq V_{out}' R$$

$$R_L \geq \frac{V_{out}'}{V - V_{out}'} R$$

HW: Derive current driver to add to circuit.


NAND-DIODE TRANSISTOR LOGIC

NAND

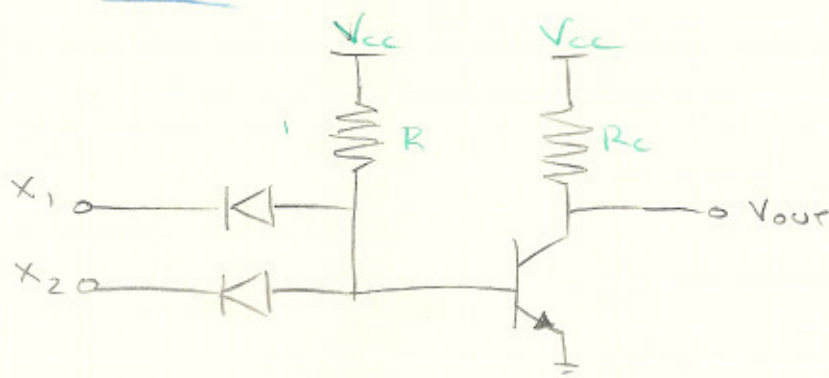

GIVEN: V_{cc} , $I_{cc(sat)}$, $V_{CE(sat)}$, β , $V_{BE(T)}$, V_{in}^0 , R_i
 $(V_{cc} - V_{in}^0) < V_{TD}$

ANALYSIS: worst case scenario

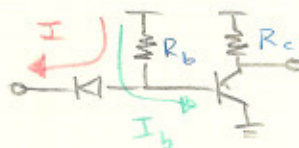

when T_1 is in saturation mode ($I_p = 0$)

$$R_C I_{SAT} + V_{CE(SAT)} = V_{CC}$$

$$R_C = \frac{V_{CC} - V_{CE(SAT)}}{I_{C(SAT)}}$$

$$V_{CC} = I_B R_B + V_{BE(T)}$$

$$I_B = \frac{V_{CC} - V_{BE(T)}}{R_B}$$

$$I_B \geq I'_B = \frac{I_{C(SAT)}}{\beta}$$

$$\frac{V_{CC} - V_{BE(T)}}{R_B} \geq \frac{I_{C(SAT)}}{\beta}$$

$$R_B \leq \frac{V_{CC} - V_{BE(T)}}{I_{C(SAT)}} \cdot \beta$$

when transistor is in cut off mode.

$$V_{BE} < V_{BE(T)}$$

$$I R_B + I R_D + I R_i + V_{TD} + V_{in}^0 = V_{CC}$$

$$I = \frac{V_{CC} - V_{in}^0 - V_{TD}}{R_B + R_D + R_i}$$

$$V_{BE} = V_{CC} - I R_B$$

$$V_{CC} - I R_B < V_{BE(T)}$$

$$V_{CC} - \frac{V_{CC} - V_{TD} - V_{in}^0}{R_B + R_D + R_i} R_B < V_{BE(ON)}$$


$$V_{CC} - V_{BE(ON)} < \frac{V_{CC} - V_{TD} - V_{in}^0}{R_B + R_D + R_i} R_B$$

$$R_i (V_{CC} - V_{BE(ON)}) + (R_B + R_D)(V_{CC} - V_{BE(ON)}) < (V_{CC} - V_{TD} - V_{in}^0) R_B$$

$$R_i (V_{CC} - V_{BE(ON)}) < (V_{CC} - V_{TD} - V_{in}^0) R_B - (R_B + R_D)(V_{CC} - V_{BE(ON)})$$




$$R_i < \frac{(V_{CC} - V_{TD} - V_{in}^0) R_B - (R_B + R_D)(V_{CC} - V_{BE(ON)})}{V_{CC} - V_{BE(ON)}}$$

Solution

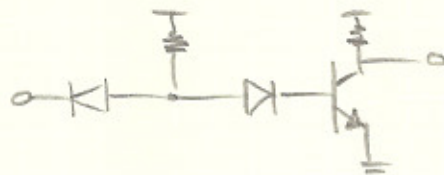


$$V_{BE(ON)} = V_{BE(ON)} + V_{TD}'$$

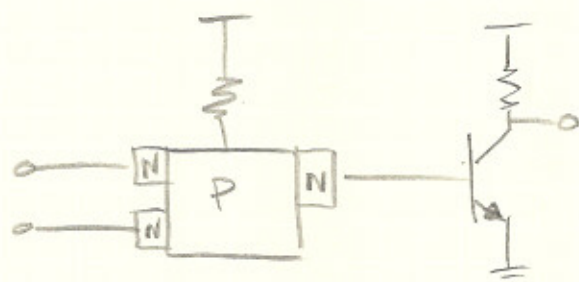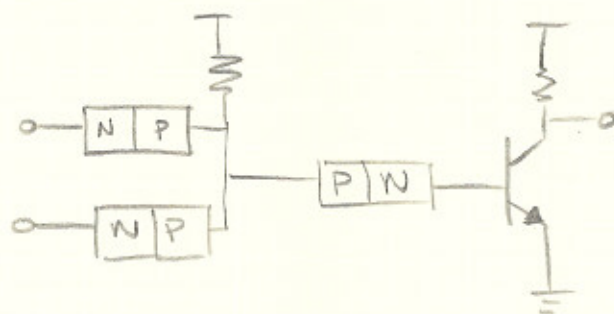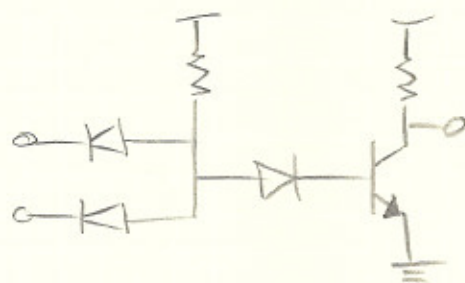HW: Redirive, and derive for current driver.



$$w_p < l_n$$

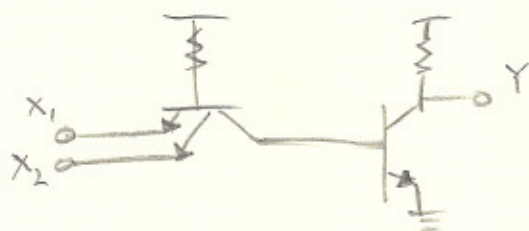

$$Y = \overline{X_1 \cdot X_2}$$

