
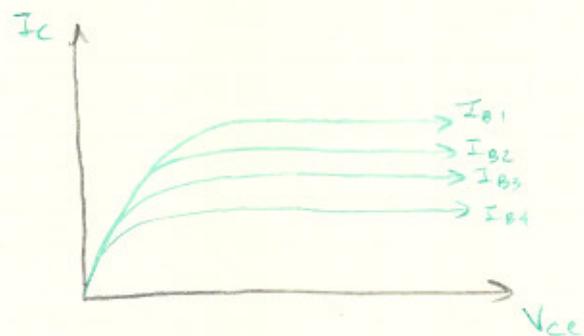



$$V_{ce} = V_{cc} - I_c R_c$$

when
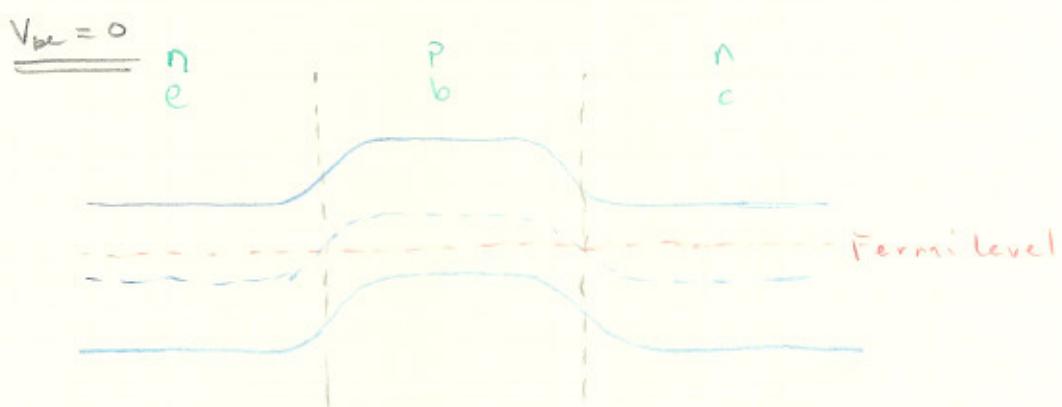
$$V_{be} \uparrow \rightarrow I_E \uparrow \rightarrow I_c \uparrow \rightarrow V_{ce} \downarrow$$





$V_{be} > V_{beT}$

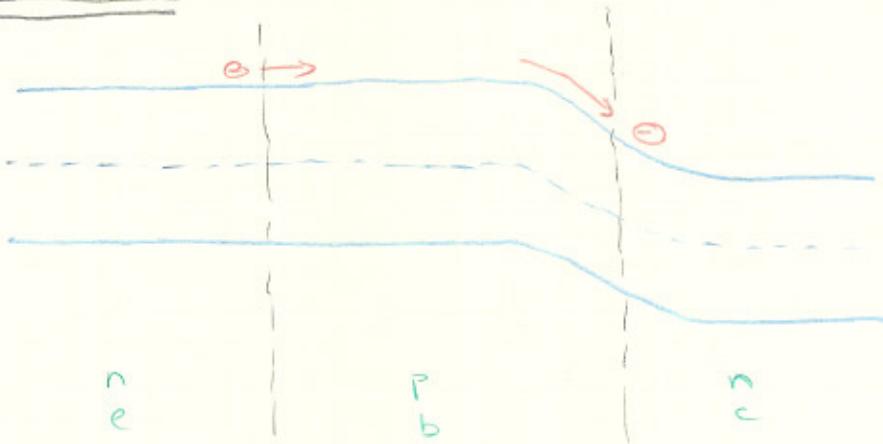


Note: In reality when an electric field is placed on the crystal, the energy band diagram is really not a shape.




### SATURATION MODE

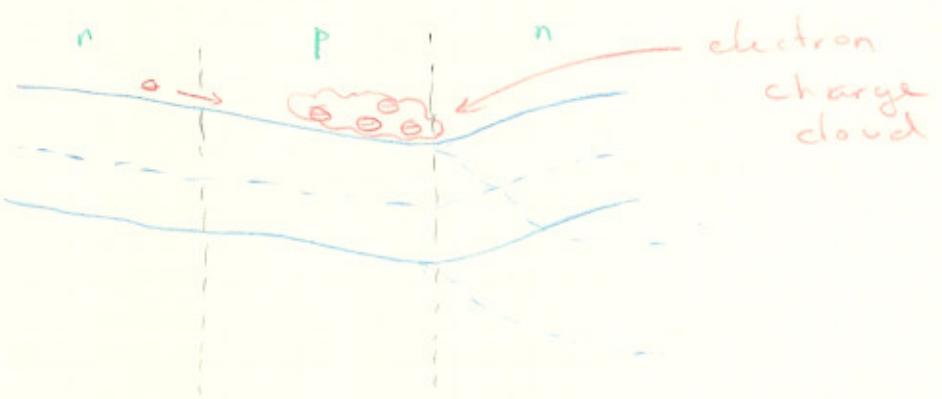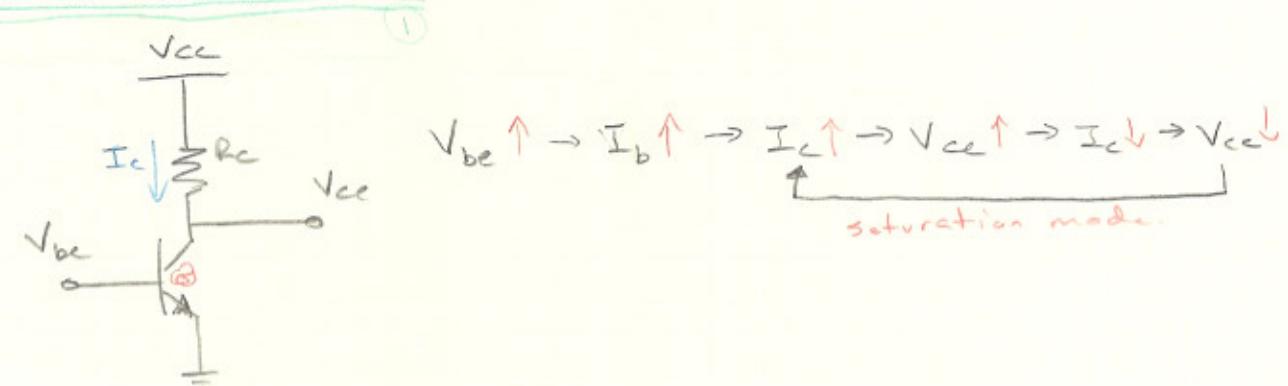

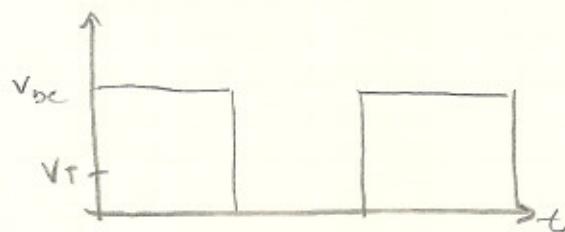Note: In saturation, an increase in  $I_B$  does not result in an increase  $I_C$ , however a charge cloud forms in the base.



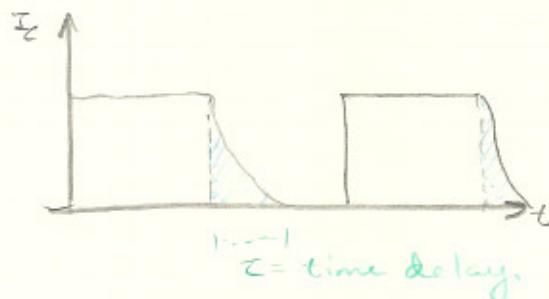note: It takes time to dissipate the electron cloud,



### FUNCTION OF COMMON Emitter.

- Saturation mode


high input  $\rightarrow$  low output

- cut off mode

low input  $\rightarrow$  high output.
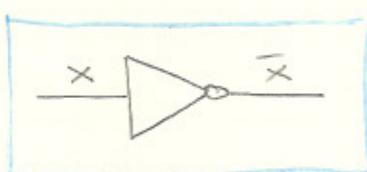
### LOGIC

the common emitter is a good example of an inverter. (NOT)




note: Symbols for logic

NOT -  
AND :  
OR +

LOGIC

	Positive	Negative
negative voltages		
positive voltages.		

we will focus on this

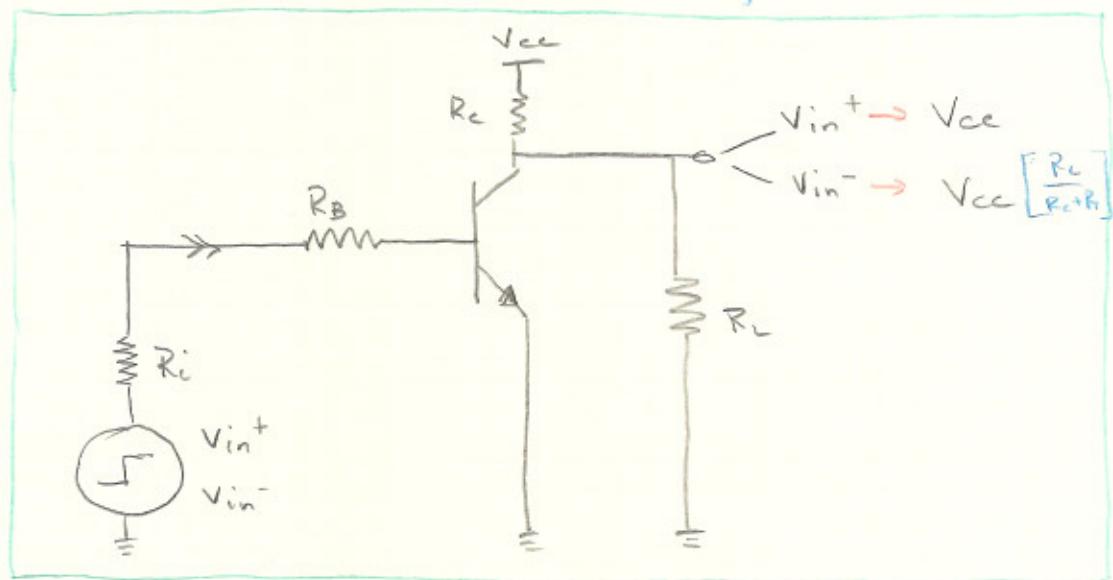

Given:  $V_{cc}$ ,  $\beta$ ,  $V_{BE\tau}$ ,  $V_{out^+}$ ,  $V_{ce}$