

COMPLEX CMOS

$$Y = (X_1(X_2 \cdot X_3 + X_4) + X_2)X_5 + X_4 \cdot X_6$$

pmos

nmos

