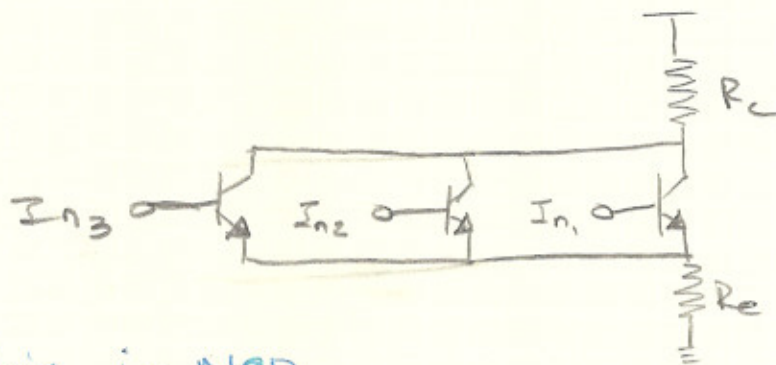



note: negative feedback reduces electron cloud, it virtually does not occur.



this is NOR



$$Y = \overline{x_1 + x_2 + \dots}$$

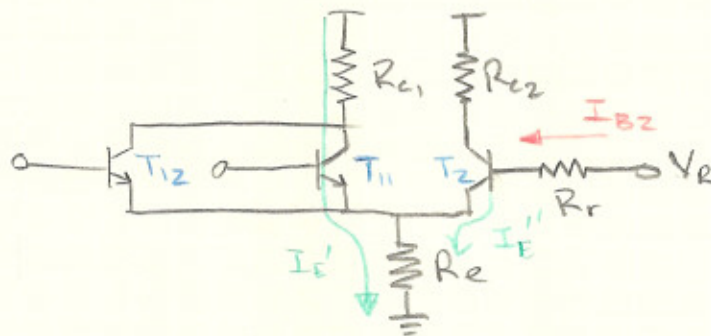

to design, we should consider only one branch.

2

GIVEN:  $V_{CC}, V_{out}, V_{in}^o, V_{in}^i, R_i, V_r, R_r$   
 $V_{BE(T)1}, V_{BE(T)2}, \beta_1, \beta_2$ .

FIND:  $R_{c1}, R_{c2}, R_e$ .

ANALYSIS:

$$V_{in}^o < V_{BE(T)1} + V_e$$

$$V_e > V_{in}^o - V_{BE(T)1}$$

$$\beta_2 I_{B2} = I_{C2}$$

$$I_{C2} + I_{B2} = I_{E2}$$

$$I_{B2} = \frac{I_{E2}}{1 + \beta_2}$$

$$I_{B2} R_r + V_{BE(T)2} + I_{E2} R_e = V_r$$

$$\frac{I_{E2}}{1 + \beta_2} R_r + V_{BE(T)2} + I_{E2} R_e = V_r$$

$$I_{E2} R_e = V_r - V_{BE(T)2} - \frac{I_{E2}}{1 + \beta_2} R_r = V_{e2}$$

$$V_{in}^o - V_{BE(T)1} < V_r - V_{BE(T)2} - \frac{I_{E2}}{1 + \beta_2} R_r$$

$$\frac{I_{E2}}{1 + \beta_2} R_r < V_r + V_{BE(T)1} - V_{BE(T)2} - V_{in}^o$$

$$0 < I_{E2} < \frac{V_r + V_{BE(T)1} - V_{BE(T)2} - V_{in}^o}{R_r} (1 + \beta_2)$$

$$V_{e2} = R_e I_{E2}$$

$$V_{e2} = R_e \frac{V_r + V_{BE(T)1} - V_{BE(T)2} - V_{in}^o}{R_r} (1 + \beta_2)$$

$$V_{in'} > V_{BE1} + V_{e2}$$

$$V_{in'} > V_{BE1} + R_e \frac{V_r + V_{BET1} - V_{BET2} - V_{in''}}{R_r} (1 + \beta_2)$$

$$R_e' = R_e < \frac{V_{in'} - V_{BET2}}{V_r - V_{BET2} + V_{BET1} - V_{in''}} \cdot \frac{R_r}{1 + \beta_2}$$

now determining  $R_{e1}$

$$I_{B1} R_i + V_{BET1} + I_{E1} R_e' = V_{in'}$$

$$I_{C1} + I_{B1} = I_{E1}$$

$$\frac{I_{C1}}{\beta_1} = I_{B1}$$

$$I_c \left(1 + \frac{1}{\beta_1}\right) = I_{E1} \Rightarrow I_{C1} = \frac{\beta_1 I_{E1}}{1 + \beta_1}$$

$$\frac{I_{C1}}{\beta_1} R_i + V_{BET1} + \frac{1 + \beta_1}{\beta_1} I_{C1} R_e' = V_{in'}$$

$$I_{C1} \left( \frac{R_i}{\beta_1} + \frac{1 + \beta_1}{\beta_1} R_e' \right) = V_{in'} - V_{BET1}$$

$$I_{C1} = \frac{\beta_1 (V_{in'} - V_{BET1})}{R_i + (1 + \beta_1) R_e'}$$

$$V_{out''} = V_{cc} - R_{C1} I_{C1}$$

$$R_{C1} = \frac{V_{cc} - V_{out''}}{I_{C1}} = \frac{(V_{cc} - V_{out''})(R_i + (1 + \beta_1) R_e')}{\beta_1 (V_{in'} - V_{BET1})}$$

$$I_{B2} R_r + V_{BET2} + R_e' \cdot I_{E2} = V_r$$

$$\frac{I_{C2}}{\beta_2} R_r + V_{BET2} + R_e' \frac{1 + \beta_2}{\beta_2} I_{C2} = V_r$$

$$I_{c2} = \frac{(V_r - V_{BE2})(B_2)}{R_r + (1 + B_2)R_{e'}}$$

$$V_{c2} + R_{c2}I_{c2} = V_{cc}$$

$$R_c = \frac{V_{cc} - V_{c2}}{I_{c2}} = \frac{(V_{cc} - V_{c2})(R_r + (1 + B_2)R_{e'})}{(V_r - V_{BE2})B_2}$$