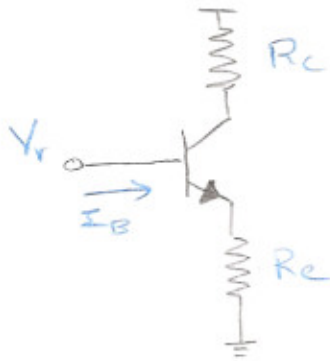


If you have a constant current through A varying resistance then the voltage also varies.



$$I_e R_e + V_{BE} = V_r$$

$$I_e = \frac{V_r - V_{BE}}{R_e}$$

$$I_c = \alpha I_e$$

$$I_c = \frac{1}{R_e} (V_r - V_{BE}) \alpha$$


$$I_c = \frac{1}{R_e} [\text{constant}]$$

∴ if  $R_e$  is constant  $I_c$  is constant


$I_c$  is independent of  $R_c$

This circuit is a current generator for Load  $R_c$

### INTEGRATED INJECTED LOGIC

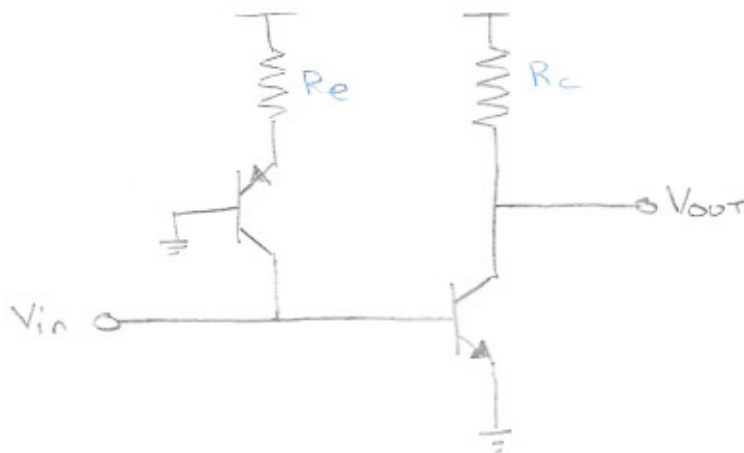

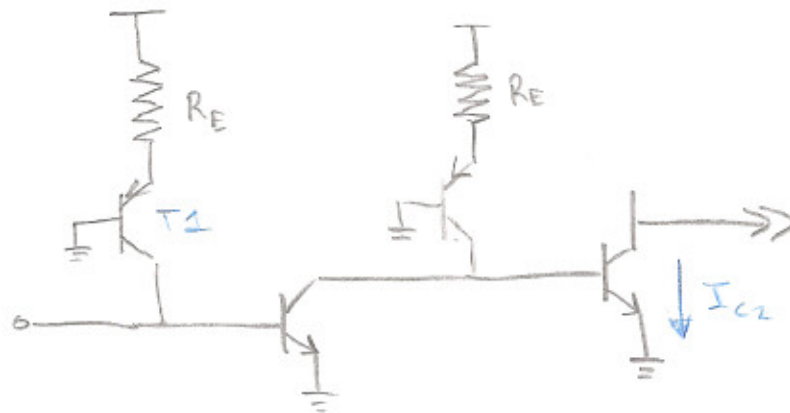note: If connecting to another cell we do not need  $R_c$



GIVEN:  $\alpha$ ,  $V_{CC}$ ,  $I_{C2}(\text{SAT})$ ,  $V_{BE1}$

FIND:  $R_E$  =

ANALYSIS:  $I_E R_E + V_{BE1} = V_{CC}$   
 $R_E = \frac{V_{CC} - V_{BE1}}{I_{E1}}$

$$I_{E1} = I_{C1} / \alpha_1 \quad \therefore \quad R_E = \frac{\alpha_1 (V_{CC} - V_{BE1})}{I_{C1}}$$



note: The input of the second stage is equal to the output of the first stage

$$\therefore I_{C1} = I_{B2} = I_{C2}(\text{SAT})$$

$$R_E = \left( \frac{V_{CC} - V_{BE1}}{I_{C2}(\text{SAT})} \right) \alpha_1$$

Consider multiple connectors, if we cascade 4 cells and share  $R_E$

$$R_{E'} = R_E / 4$$

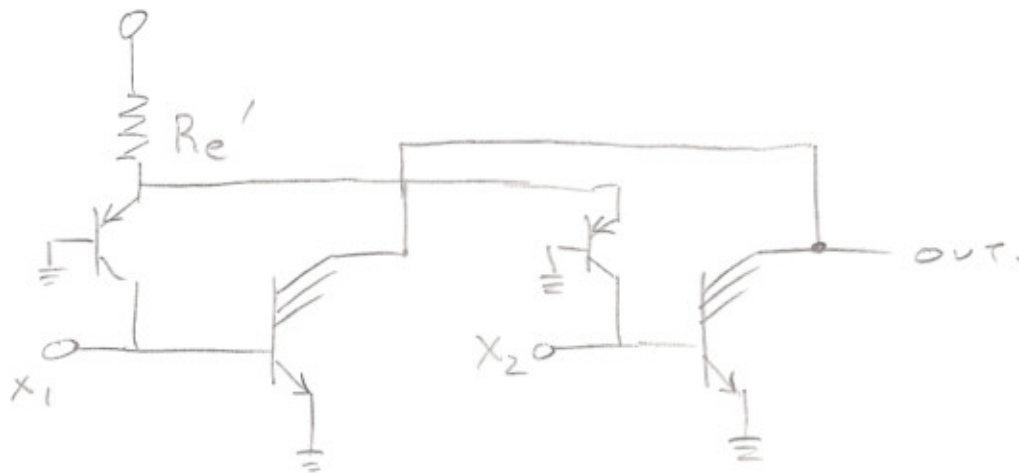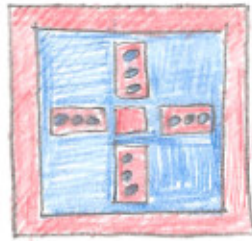

Consider connecting collectors

$X_1$	$X_2$	OUT
0	0	1
0	1	0
1	0	0
1	1	0

note: This is a NOR gate that accomodate any design.