
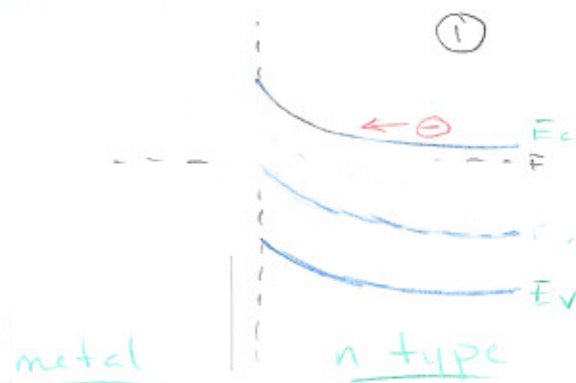


SCHOTKY DIODE

$$\ell_p > \ell_m$$

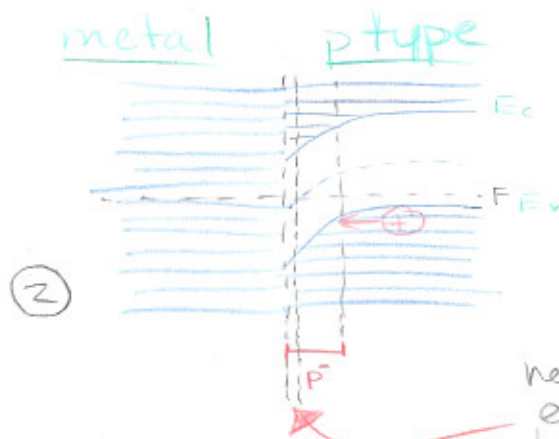


note: here we have created an energy barrier as well.

here if the middle of the energy band gap drops below the fermi level then n type can form.

when


$$\ell_p < \ell_m$$

metal | p type

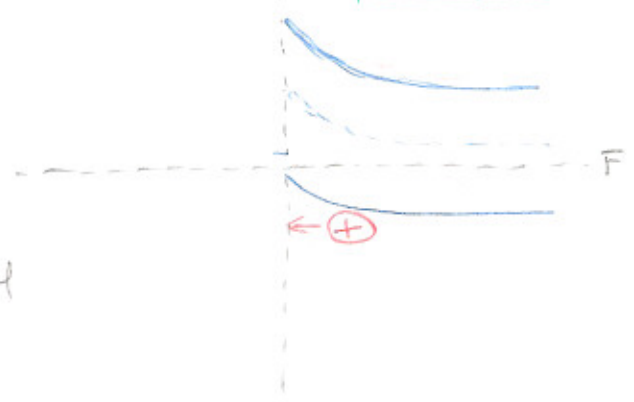


note: no energy barrier


RE: ①:

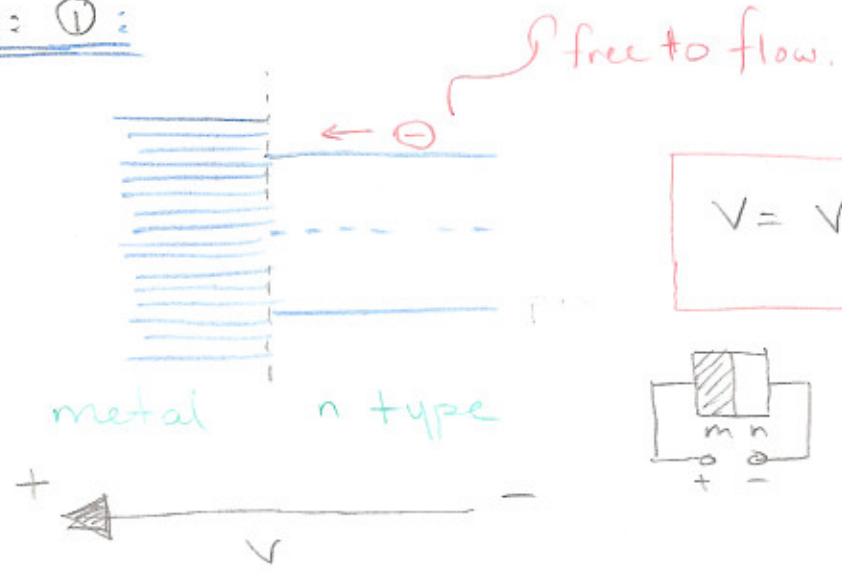


$$V = V_T = \frac{\Delta \phi}{q_0}$$

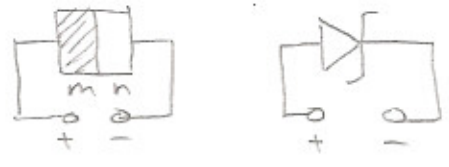



RE: ②:

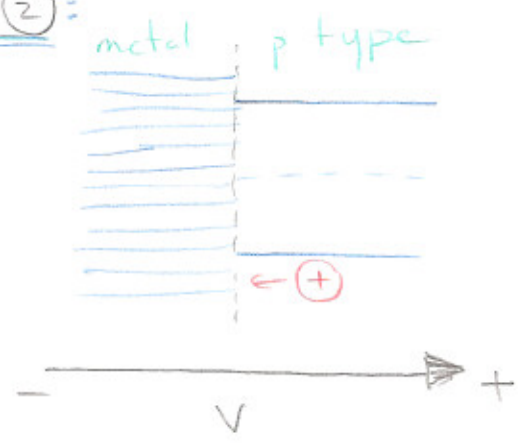

$$V = V_T = \frac{\Delta \phi}{q_0}$$

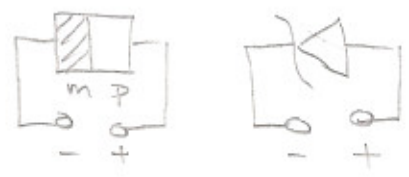

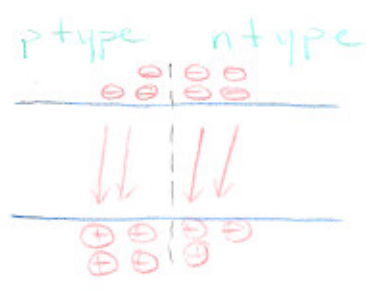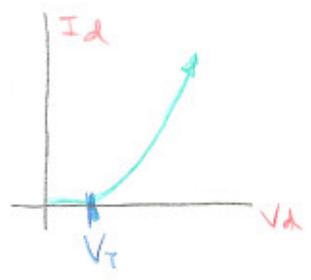
note: the advantages are lower threshold voltage and faster switching time.



note: there is a time delay for the recombination. ( $\tau$ )

the schottky diodes do not have this ( $\tau$ ) is can be assumed  $\tau \approx 0$ .

# LOGIC CIRCUITS

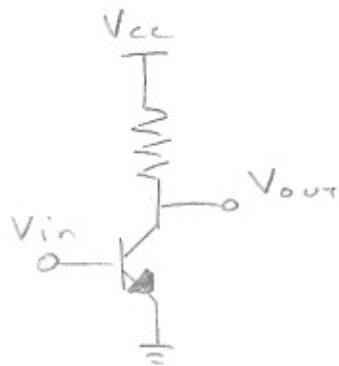


NOT



$$Y = \overline{X}$$


OR

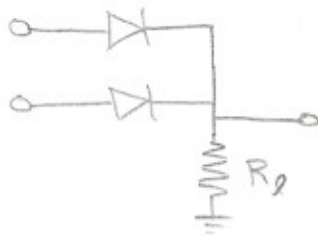

$$Z = X + Y$$

$$V_{in} < V_T(D)$$

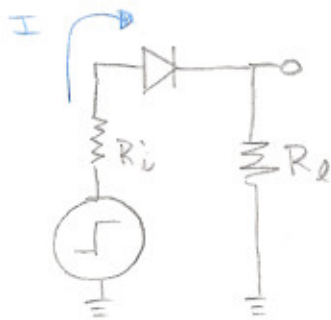note: in design of this circuit we should take into account  $V_T$  and  $R_i$  of diode.



GIVEN:  $V_{in}', R_i, V_{out}', V_{TD}, R_D$

FIND:  $R_l$

ANALYSIS:

$$IR_i + IR_D + IR_l + V_{TD} = V_{in}'$$

$$I = \frac{V_{in}' - V_{TD}}{R_i + R_D + R_l}$$

$$V_{out} = IR_l > V_{out}'$$


$$R_l \frac{V_{in}' - V_{TD}}{R_i + R_D + R_l} > V_{out}'$$

$$R_L (V_{in}' - V_{TD}) > V_{out}' R_L + V_{out}' R_D + V_{out}' R_i$$

$$R_L (V_{in}' - V_{TD} - V_{out}') > V_{out}' (R_D + R_i)$$


$$R_L > \frac{V_{out}' (R_D + R_i)}{V_{in}' - V_{TD} - V_{out}'}$$

AND:

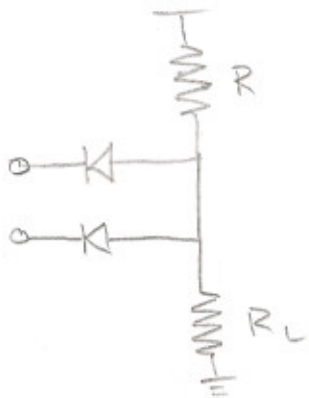

$$z = x \cdot y$$

for design we should consider.

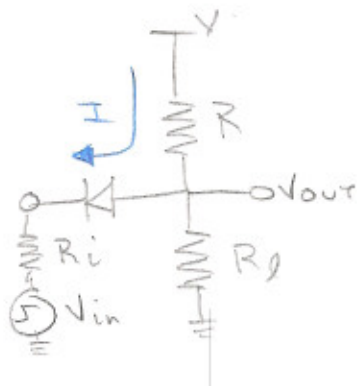

GIVEN:  $V, V_{in}^0, R_i, V_{TD}, R_D$

FIND:  $R, R_L$

ANALYSIS:

if  $I \neq 0$ ,  $I_L \approx 0$

$$IR + IR_D + IR_i + V_{TD} + V_{in}^0 = V$$

$$V_{out} = V - IR \leq V_{in}^0$$

$$V - \frac{V - V_{in}^0 - V_{TD}}{R + R_D + R_i} \cdot R \leq V_{in}^0$$