

EX:

$$V_f = 240 \text{ V}$$

$$V_a = 240 \text{ V}$$

$$P = 12 \text{ HP}$$

$$R_a = 0.28 \Omega$$

$$L_a = 2.81 \text{ mH}$$

$$R_f = 320 \Omega$$

$$L_f = 2 \text{ H}$$

$$K_e = 1.03$$

$$J = 0.087 \text{ kg}\cdot\text{m}$$

$$D = 0.02 \text{ Nms}$$

$$\tau_L = 15 \text{ Nm}$$

@ $t=0$, V_f drops to 192V

Find: $\omega(t)$, $i_f(t)$, $i_a(t)$

SOL: Step 1 determine initial conditions
 $i_f(0)$, $i_a(0)$ & $\omega(0)$

$$i_f = \frac{V_f}{R_f} = \frac{240}{320} = 0.75 \text{ A}$$

$$V_a = R_a i_a + K_e i_f \omega$$

$$K_e i_f i_a - \tau_L - D\omega = 0$$

$$\therefore i_a = \frac{V_a}{R_a} - \frac{K_e i_f \omega}{R_a}$$

$$\frac{K_e i_f V_a}{R_a} - \frac{(K_e i_f)^2 \omega}{R_a} - \tau_L - D\omega = 0$$

$$\omega = \frac{K_e i_f V_a - R_a \tau_L}{(K_e i_f)^2 + R_a D}$$


$$\omega = 300.8 \text{ rad/s}$$

$$i_a = 27.2 \text{ A}$$

$$I_f(s) = \frac{V_f(s) - L_f \dot{i}_f(0)}{L_f s + R_f}$$

$$V_a(s) = \frac{240}{s}$$

$$Z_L(s) = \frac{15}{s}$$

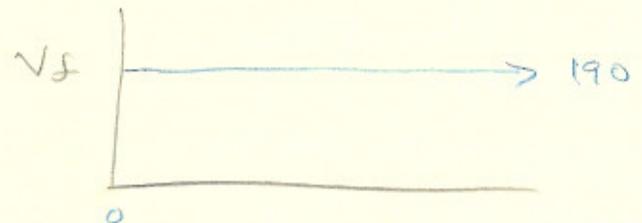

$$I_f(s) = \frac{\frac{192}{s} + 2 \times 0.75s}{2s + 320}$$

$$= \frac{0.75s + 96}{s(s+160)}$$



$$= \frac{0.6}{s} + \frac{0.15}{s+160}$$

$$\dot{i}_f(t) = 0.6 + 0.15e^{-160t}$$

$$\omega(s) = \frac{K_e I_f (V_a(s) + L_a \dot{i}_a(0)) + (L_a s + R_a)(J\omega(0) - T)}{(Js + D)(L_a s + R_a) + (K_e I_f)^2}$$

$$= \frac{371.92}{s} - \frac{95.27}{(s+19.79)} + \frac{24.15}{(s+80.08)}$$

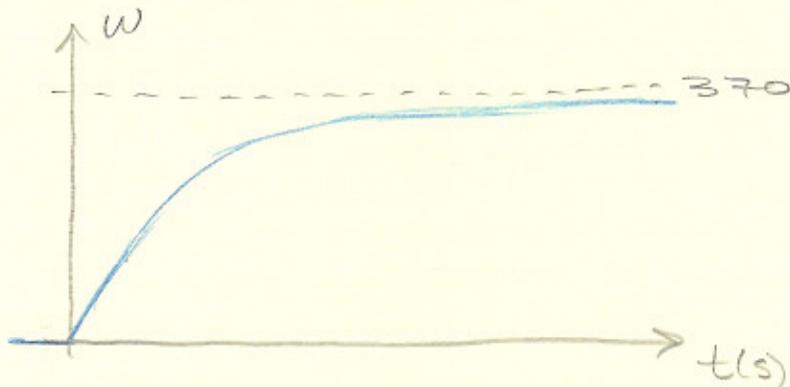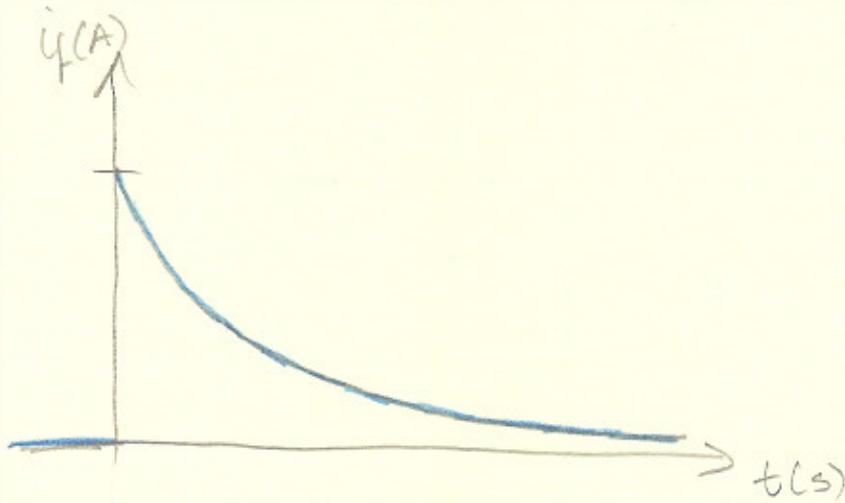
$$\omega(t) = 371.92 - 95.27e^{-19.79t} + 24.15e^{-80.08t}$$



$$I_a(s) = \frac{(V_a(s) + L a \dot{a}(0)) (J s + D) - K_e i_f (J \omega(s) - \tau_L(s))}{s}$$

$$i_f(s) = \frac{36.31}{s} + \frac{262.37}{s + 19.79} - \frac{271.48}{s + 80.08}$$
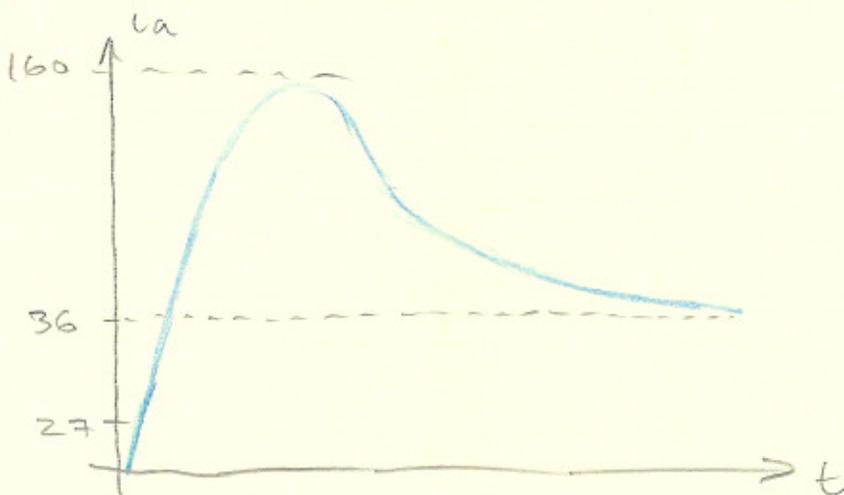
$$i_f(t) = 36.31 + 262.37 e^{-19.79t} - 271.48 e^{-80.08t}$$



$$\frac{di_a}{dt} = 0$$

$$262.37(-19.79)e^{-19.79t} - 271.48(-8008)e^{-8008t} = 0$$

$$t = 0.023 \text{ ms}$$

$$i_a(0.023) = 160 \text{ A}$$

Input $V_f(t) = R_f i_f(t) + L_f \frac{di_f(t)}{dt}$

Input $V_a(t) = R_a i_a(t) + L_a \frac{di_a(t)}{dt} + e(t)$

Disturbance

$$\tau_d(t) - \tau_l(t) - D\omega(t) = J \frac{d\omega(t)}{dt}$$

$$\tau_a(t) = K_e i_f(t) \omega(t)$$

$$\tau_d(t) = K_e i_f(t) i_a(t)$$

Hall effect Current Sensor or Resistor

$$\omega(s) = \frac{K_e I_f (V_a(s) + L_a i_a(0)) + (L_a s + R_a)(J\omega(0) - \tau_l(s))}{(J s + D)(L_a s + R_a) + (K_e I_f)^2}$$


$$\begin{aligned} i_f(t) &= I_f \\ v_a(0) &= 0 \\ \omega(0) &= 0 \end{aligned}$$

$$= \frac{K_e I_f}{(J s + D)(L_a s + R_a) + (K_e I_f)^2} V_a(s) - \frac{(L_a s + R_a)}{(J s + D)(L_a s + R_a) + (K_e I_f)^2} \tau_l(s)$$

$$w(s) = G_{Va} \rightarrow w(s) Va(s) + G_{TL} \rightarrow w(s) TL(s)$$

Poles are at the roots of the char equ.

$$(Js + D)(Las + Ra) + (Ke If)^2 = 0$$

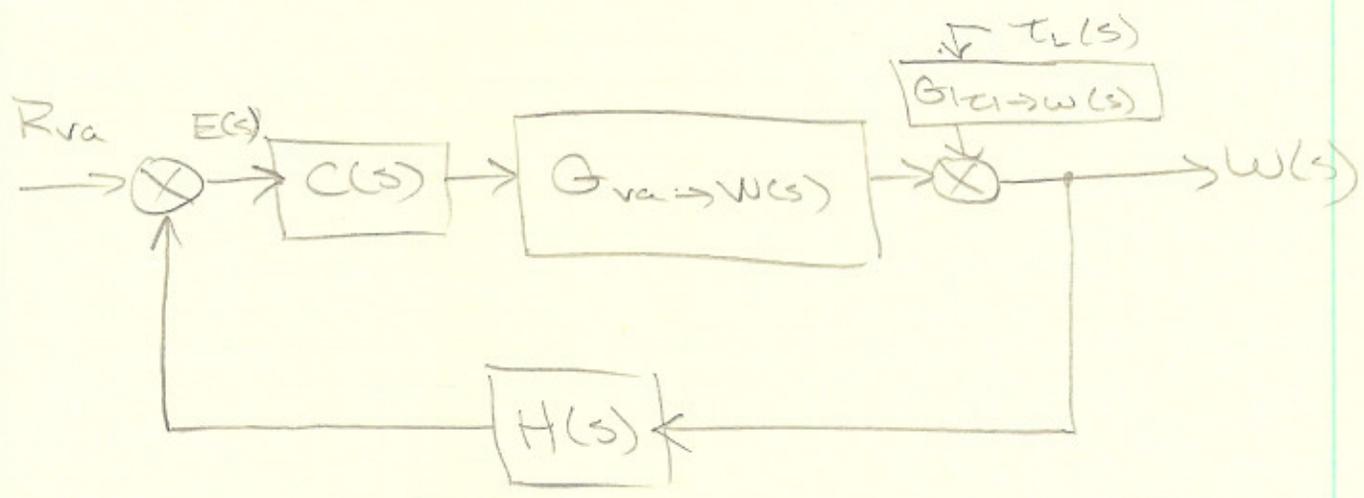

C(s) is PID.