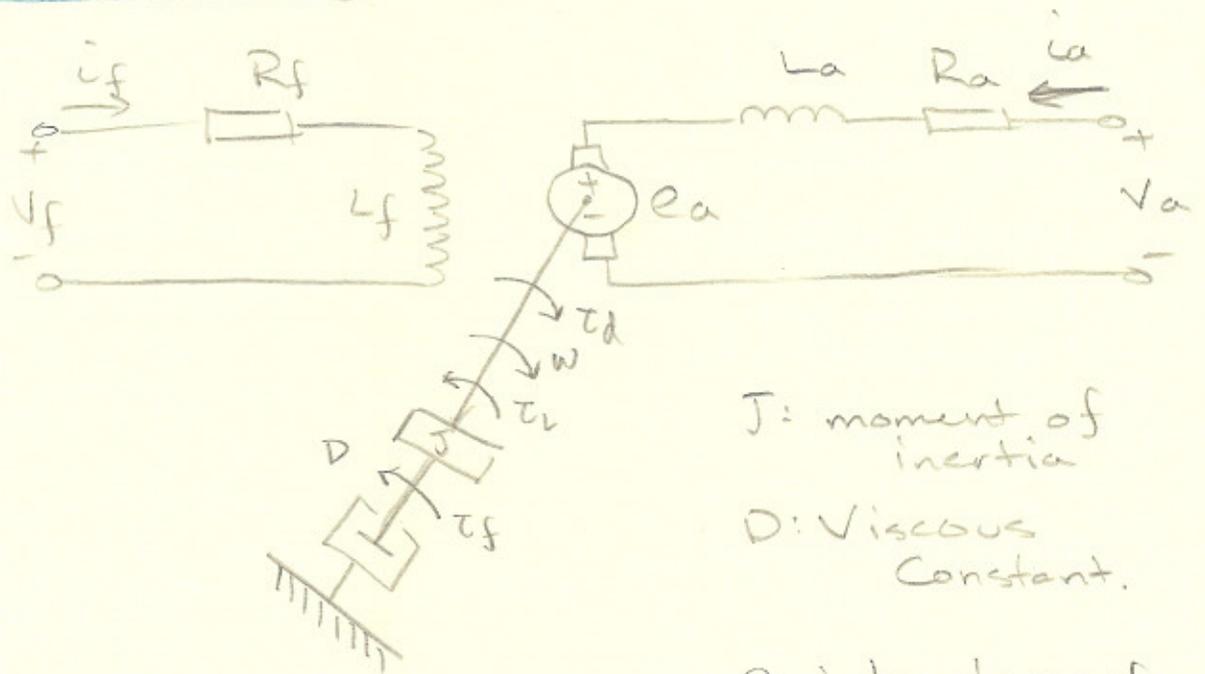


Midterm Oct 30th Ch 1 → 3

DC Motor Dynamics



J : moment of inertia

D : Viscous Constant.

e_a : back emf.

$$\tau_f = D\omega$$

By KVL

$$V_f = R_f i_f + L_f \frac{di_f}{dt}$$

$$V_a = R_a i_a + L_a \frac{di_a}{dt} + e_a$$

By Newtons Law

$$\tau_d - \tau_L - \tau_f = J \frac{d\omega}{dt}$$

$$e_a = k_e i_f \omega \quad \text{Voltage constant.}$$

$$\tau_d = k_\tau i_f i_a \quad \text{Torque constant}$$

$$i_f = i_f(t)$$

$$i_a = i_a(t)$$

$$\omega = \omega(t)$$

$$v_f = v_f(t)$$

$$v_a = v_a(t)$$

$$\tau_L = \tau_L(t)$$

functions of time.

Steady State Operation.

$$\frac{di_f}{dt} = 0 \quad \frac{di_a}{dt} = 0 \quad \frac{d\omega}{dt} = 0$$

$$\therefore v_f = R_f i_f$$

$$v_a = R_a i_a + e_a$$

$$\tau_d - \tau_L - \tau_f = 0$$

$$e_a = k_e i_f \omega$$

$$\tau_d = k_z i_f i_a$$

$$\frac{di_f(t)}{dt} = -\frac{R_f}{L_f} i_f(t) + \frac{v_f(t)}{L_f}$$

$$\frac{di_a(t)}{dt} = -\frac{R_a}{L_a} i_a(t) - \frac{k_e}{L_a} i_f(t) \omega(t) + \frac{v_a}{L}$$

$$\frac{d\omega(t)}{dt} = \frac{k_e}{J} i_f(t) i_a(t) - \frac{\tau_L(t)}{J} - \frac{D}{J} \omega(t)$$

$\mathcal{L} \rightarrow$ yields.

$$s I_f(s) - i_f(0) = \frac{R_f}{L_f} I_f(s) + \frac{1}{L_f} V_f(s)$$

$$(L_f s + R_f) I_f(s) = V_f(s) + L_f i_f(0)$$

$$I_f(s) = \frac{V_f(s) + L_f i_f(0)}{L_f s + R_f}$$

Armature - Controlled DC motor:

Assume $i_f(t) = i_f$ (constant)

$$I_f = \frac{V_f}{R_f}$$

$$\therefore L_a \frac{di_a(t)}{dt} = -R_a i_a(t) - K_e I_f \omega(t) + v_a(t)$$

$$L_a s I_a(s) - L_a i_a(0) = -R_a I_a(s) - K_e I_f \omega(s) + V_a(s)$$

$$I_a(s) = \frac{[V_a(s) + L_a i_a(0)] + K_e I_f \omega(s)}{s L_a + R_a}$$

$$J s \omega(s) - J \omega(0) = K_e I_f I_a(s) - \tau_L(s) - D \omega(s)$$

$$(J s + D) \omega(s) = K_e I_f I_a(s) + J \omega(0) - \tau_L(s)$$

$$(J s + D) \omega(s) = K_e I_f \frac{[V_a(s) + L_a i_a(0)] - K_e I_f \omega(s)}{L_a s + R_a} + J \omega(0) - \tau_L(s)$$

$$(Ls + Ra)(Js + D)w(s) = KeI_f [V_a(s) + La i_a(0) - (KeI_f)^2 w(s) + (Ls + Ra)(Jw(0) + \tau_L(s))]$$

$$w(s) = \frac{KeI_f [V_a(s) + La i_a(0)] + (Ls + Ra)(Jw(0) + \tau_L(s))}{(Ls + Ra)(Js + D) + (KeI_f)^2}$$

See Lecture Notes for more exact derivation.