

EX:

$$\begin{aligned}
 V_a &= V_f = 240\text{V} \\
 P &= 12\text{ hp} \\
 R_a &= 0.28\ \Omega \\
 L_a &= 2.81\text{ mH} \\
 R_f &= 320\ \Omega \\
 L_f &= 2\text{ H} \\
 K_e &= 1.03 \\
 J &= 0.087\text{ kg}\cdot\text{m} \\
 D &= 0.02\text{ N}\cdot\text{m}\cdot\text{s}
 \end{aligned}$$

V_a is suddenly applied at $t=0$ with no load
Find $i_a(t)$ & $\omega(t)$.

SOL

$$\begin{aligned}
 i_a(0) &= 0 \\
 \omega(0) &= 0
 \end{aligned}$$

$$\omega(s) = \frac{K_e I_f (V_a(s) + L_a i_a(0)) + (L_a s + R_a)(J\omega(0) - T_L(s))}{(Js + D)(L_a s + R_a) + (K_e I_f)^2}$$

$$= \frac{(1.03)(0.75)\left(\frac{240}{s} + 0\right) + (0.00281s + 0.28)(0 - 0)}{(0.087s + 0.02)(0.00281s + 0.28) + ((1.03)(0.75))^2}$$


$$= \frac{7.5838 \times 10^5}{s(s + 44.482)(s + 55.391)}$$

Partial fraction expansion results in

$$= \frac{307.80}{s} - \frac{1562.9}{s + 44.482} + \frac{1255.1}{s + 55.391}$$

 \mathcal{L}^{-1}
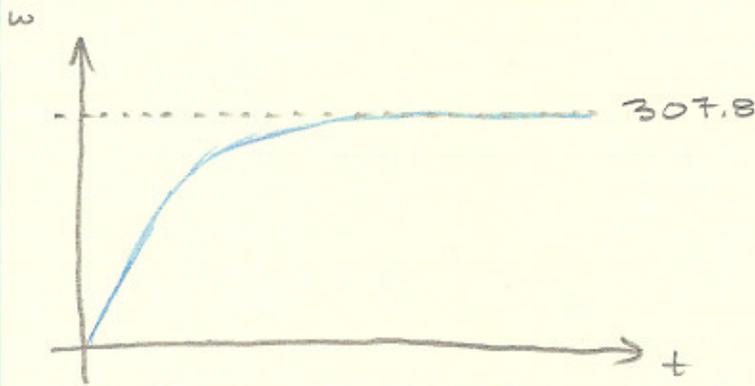
$$\omega(t) = 307.80 - 1562.9 e^{-44.482t} + 1255.1 e^{-55.391t}$$




$$I_a(s) = \frac{(V_a(s) + L_a \dot{i}_a(0))(Js + D) - K_e I_f (J\omega(0) - \tau_L(s))}{(Js + D)(Ls + R_a) + (K_e I_f)^2}$$

$$= \frac{\left(\frac{240}{s} + 0\right)(0.087s + 0.02) + 0}{(0.087s + 0.02)(0.00281s + 0.28) + (103 \times 0.75)^2}$$

$$= \frac{7.9687}{s} + \frac{7788.8}{s + 44.482} + \frac{-7796.7}{s + 55.391}$$
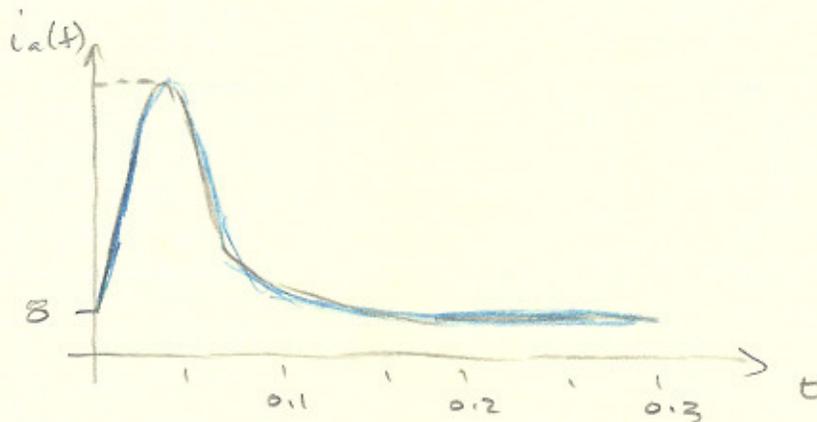
$$i_a(t) = 7.9687 + 7788.8 e^{-44.482t} - 7796.7 e^{-55t}$$



This current is way too high, V_a can not be applied all at once... we must slowly increase the voltage on the armature.

Time constants

$\tau_m = \frac{J}{D}$ (mechanical time constant)

$\tau_e = \frac{L_a}{R_a}$ (electrical time constant)

$\tau_m \gg \tau_e$


EX

- $V_a = V_s = 240V$
- $P = 12 \text{ hp}$
- $R_a = 0.28 \Omega$
- $L_a = 2.81 \text{ mH}$
- $R_f = 320 \Omega$
- $L_f = 2H$
- $K_e = 1.03$
- $J = 0.087$
- $I_a = 37.3 \text{ A}$
- $D = 0.02 \text{ N}\cdot\text{m}\cdot\text{s}$

30 V is suddenly applied at $t=0$ to load of $15 \text{ N}\cdot\text{m}$
Find $i_a(t)$ & $\omega(t)$

$i_a(0) = 0$
 $\omega(0) = 0$

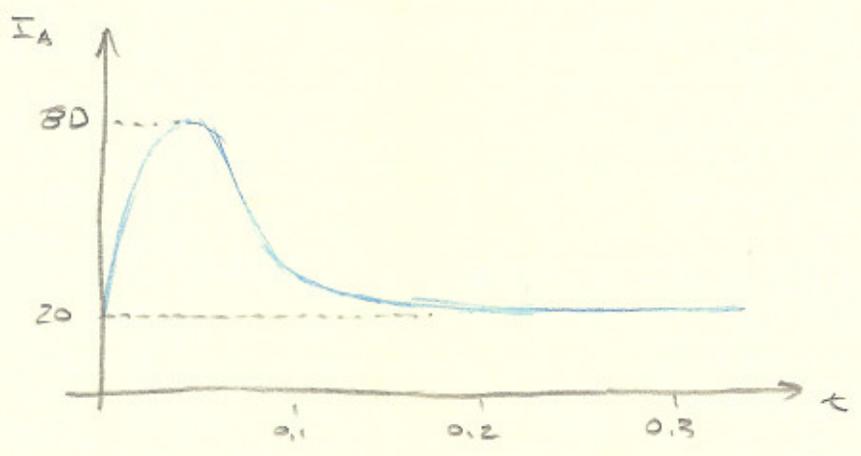$I_a = 20.234 + 875.9 e^{-44.482t} - 896.14 e^{-55.391t}$



4.
Before $t=0$, 30V has been applied to the armature winding for a long time so that it can reach steady state

At $t=0$, 60V is applied to V_a suddenly calculate $i_a(t)$, $\omega(t)$

$$i_a(0) = ?$$

$$\omega(0) = ?$$

$$V_f(\infty) = R_f I_f(\infty)$$

$$I_f(\infty) = \frac{V_f(\infty)}{R_f} = \frac{240}{320} = 0.75$$

$$V_a(\infty) = R_a i_a(\infty) + K_e I_f \omega(\infty)$$

$$K_e I_f i_a(\infty) - \tau_L(\infty) - D\omega(\infty) = 0$$

$$\left. \begin{array}{l} i_a(0) = i_a(\infty) \\ \omega(0) = \omega(\infty) \end{array} \right\} \text{ b/c we need to see what they were at 30V on } V_a.$$

$$i_a(\infty) = 20.2 \text{ A}$$

$$\omega(\infty) = 31.7 \text{ A}$$

Then we can do the rest of the calculations.

Field Control DC motors

$$\frac{di_f(t)}{dt} = -\frac{R_f}{L_f} i_f(t) + \frac{1}{L_f} V_f(t)$$

$$\frac{di_a(t)}{dt} = -\frac{R_a}{L_a} i_a(t) - \frac{K_e}{L_a} i_f(t) \omega(t) + \frac{V_a(t)}{L_a}$$

$$\frac{d\omega(t)}{dt} = \frac{K_e}{J} i_a(t) i_f(t) - \frac{1}{J} \tau_L(t) - \frac{D}{J} \omega(t)$$

With this system we assume

$$i_f(t) = I_s \quad (\text{constant})$$